



# Rewards Await ... if You Are Willing !

Jeff - KØZR



**ARRL** *The national association for  
AMATEUR RADIO*



# Some Facts About Circuit Design

- You don't need to be an engineer to do this
- Designing your first circuit can be intimidating:
  - If it works – great
  - If it does not work – *not so* great!
    - However, you will learn far more from your mistakes than all your successes
- Many amateurs today are missing out on some of the greatest satisfaction amateur radio has to offer:
  - Designing and building something electronic
- It has never been easier with the wide variety of tools available on the internet today



**ARRL** The national association for  
AMATEUR RADIO





# What Are Some of These Tools?

- For “true math” calculations, Python
  - Absolutely free: [www.python.org](http://www.python.org)
  - Beginner’s Guides found all over the internet
  - N1RM uses Python to post-process LARG Field Day data
  - W5ODJ uses Python to immediately provide azimuth headings for stations entered into his log
- L-network design for antenna matching
  - [www.daycounter.com/Calculators/L-Matching-Network-Calculator](http://www.daycounter.com/Calculators/L-Matching-Network-Calculator)
- Circuit analysis – “SPICE”
  - LT SPICE – from Linear Technology/Analog Devices
  - 5SPICE
  - PartSim
  - Simetrix - [www.simetrix.com](http://www.simetrix.com)
- This is what will be demonstrated today




**ARRL** The national association for  
AMATEUR RADIO


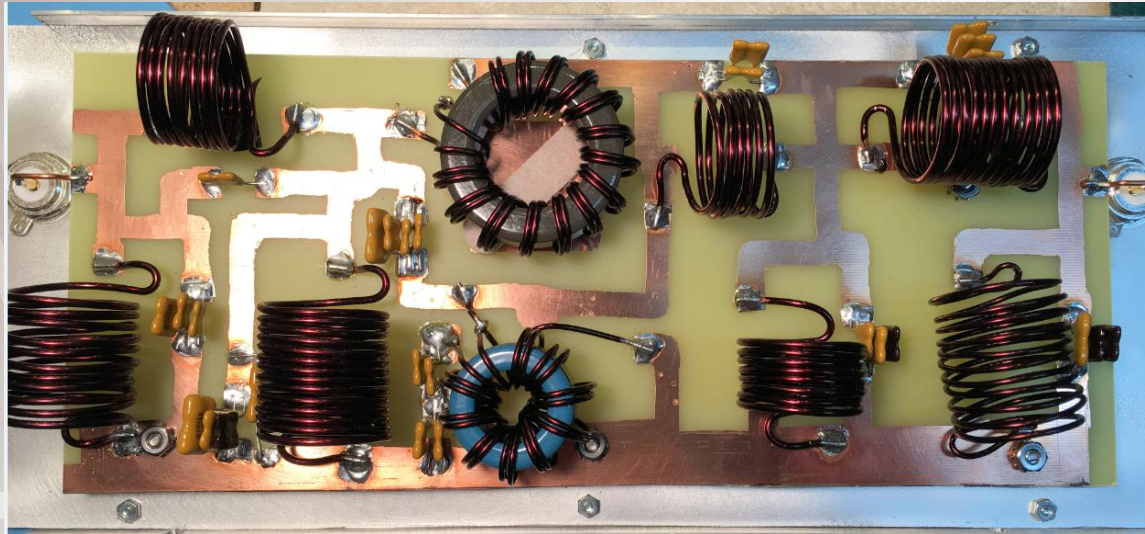
# KØZR 2 KW BPF for 80m

- Fall of 2016, I spoke about my homebrewed bandpass filters for SO2R



15"

15"

- Analysis revealed high RF current, requiring multiple, paralleled capacitors
  - Could have “painstakingly” used trial and error to determine combinations
  - Or could write a python “script” to optimally choose capacitor values from catalog values available



**ARRL** The national association for  
AMATEUR RADIO





# Python Example

- Wrote a python “script” which:
  - Chose capacitance values from standard catalog values and
    - Kept values somewhat close together to maintain optimal current sharing
    - Used a sufficient number of capacitors such that currents through each were kept below a specified maximum value

Enter Total Current, A: 12

Maximum Current in Each Capacitor, A:5

Enter Total Capacitance : 725

Requested Maximum Current Capacity = 12

>>> Minimum # of Capacitors to use is 3


#	C1	#	C2	Cap Range	Tot Cap
1	180.0	2	270.0	90.0	720.0
1	200.0	2	270.0	70.0	740.0
2	200.0	1	300.0	100.0	700.0



**ARRL** The national association for  
AMATEUR RADIO



# Simulate a BPSK Signal

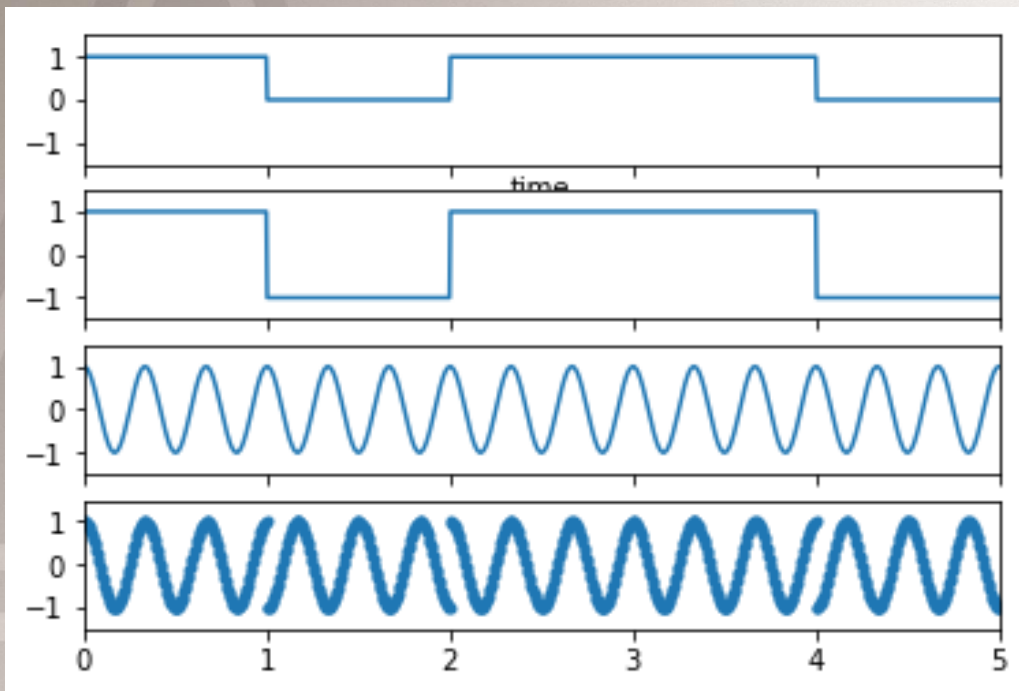

- BPSK is one of the simplest digital formats – Binary Phase Shift Keying
- “1”s and “0”s are determined by the phase of the signal
- The downloaded version of Python I use has over 500 different libraries with literally thousands of functions at your fingertips



**ARRL** The national association for  
AMATEUR RADIO





# What is SPICE?

- SPICE stands for “Simulation Program with Integrated Circuit Emphasis”
  - First release was in 1973
  - Developed at University of California at Berkeley
  - Many versions and improvements since then
    - Most visible improvements are standard Windows interfaces, etc
- With SPICE one can design passive circuits, such as matching networks, multiple-transistor amplifiers, or digital logic
  - Most SPICE versions have catalogs of parts “built-in”, thus accelerating the development of designs



**ARRL**

*The national association for*  
**AMATEUR RADIO**



# Why Simetrix?

- Of the SPICE programs mentioned earlier, Simetrix was selected here largely because this is what I use in my work environment
  - My version costs in excess of \$10,000
    - Unlimited nodes and circuit elements
    - Exhaustive component libraries
  - The free version is limited to ~ 100 elements
    - Generally exceeds most people's needs for amateur use
- I have used LTSpice and 5SPICE but they are generally not used in the professional engineering environments....




**ARRL** The national association for  
AMATEUR RADIO





# Circuit One: A Simple RC Circuit

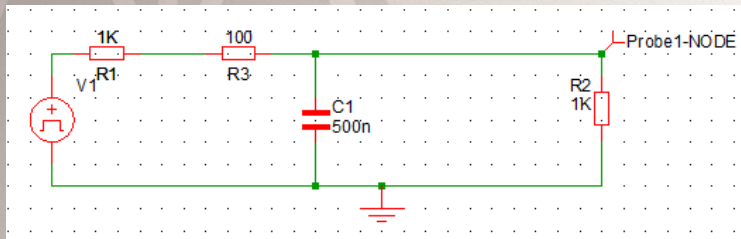


A square-wave generator  
 $f = 10 \text{ kHz}$



**ARRL** The national association for  
AMATEUR RADIO

## Input Signal


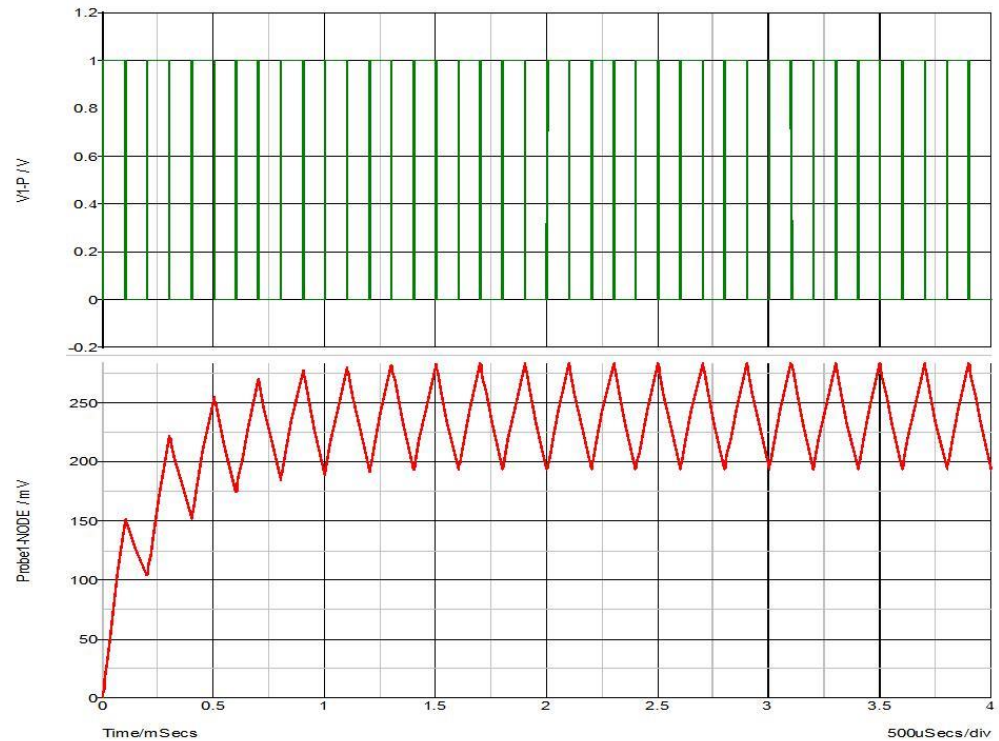


## Output Waveform

Each positive excursion of the square wave charges the capacitor more until it reaches the peak value, then it discharges until the next positive peak arrives



# Two -Transistor Oscillator

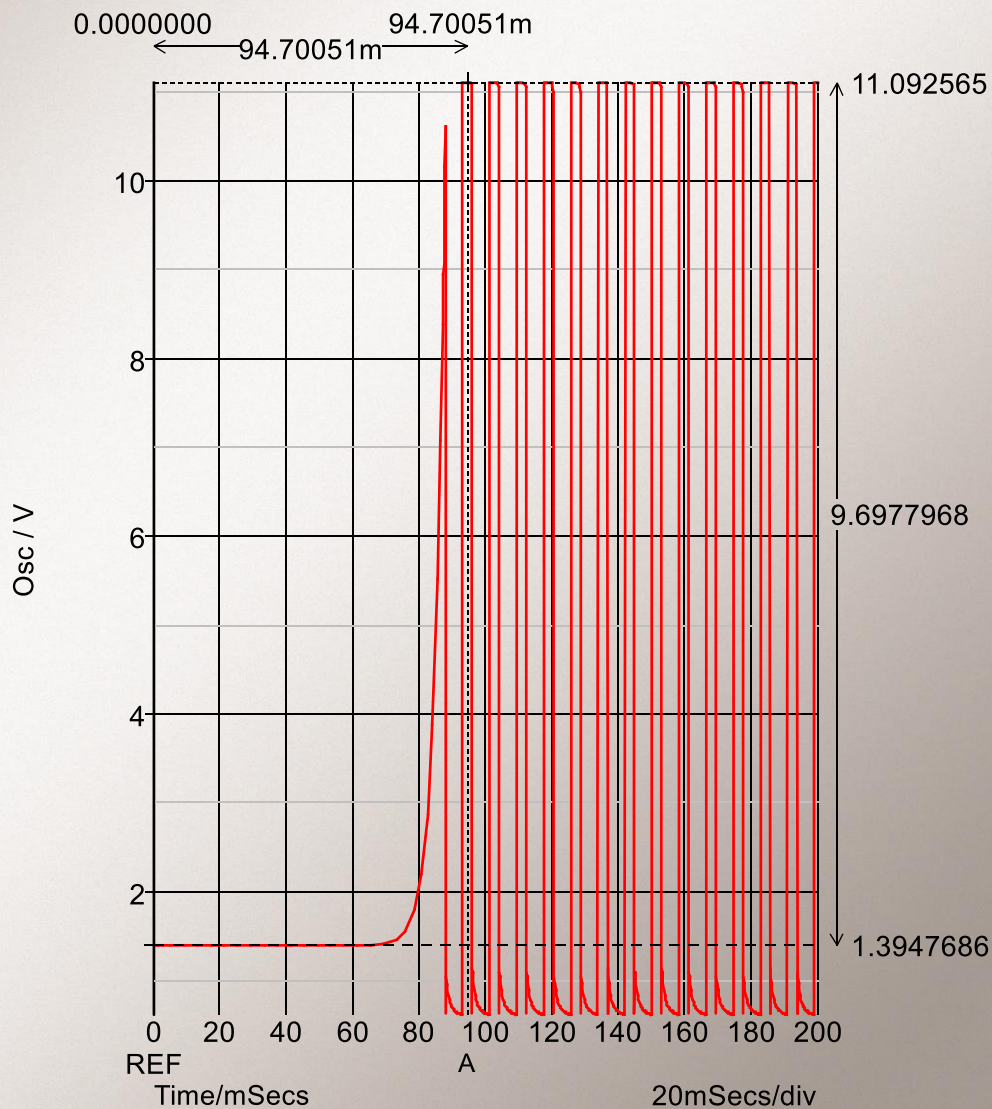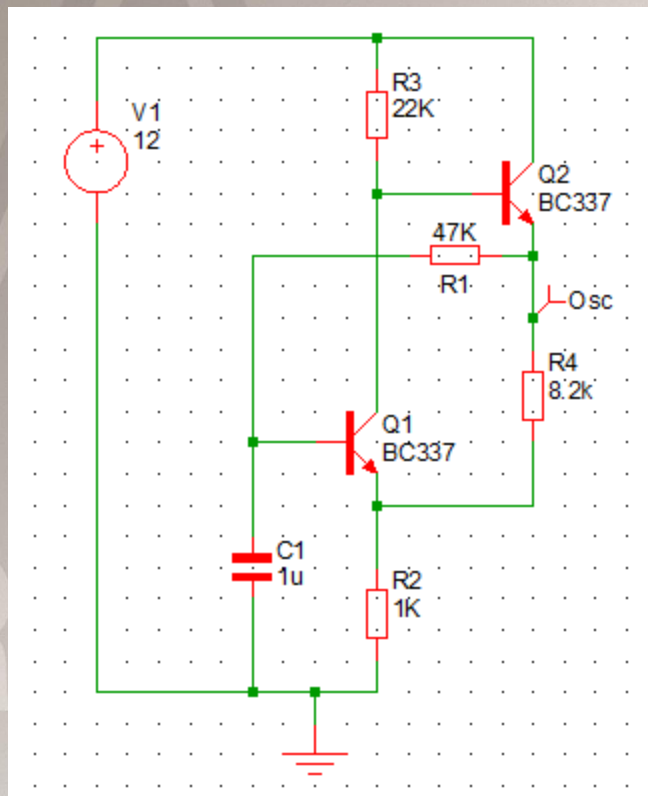


**ARRL** The national association for  
AMATEUR RADIO





# Bias Determination

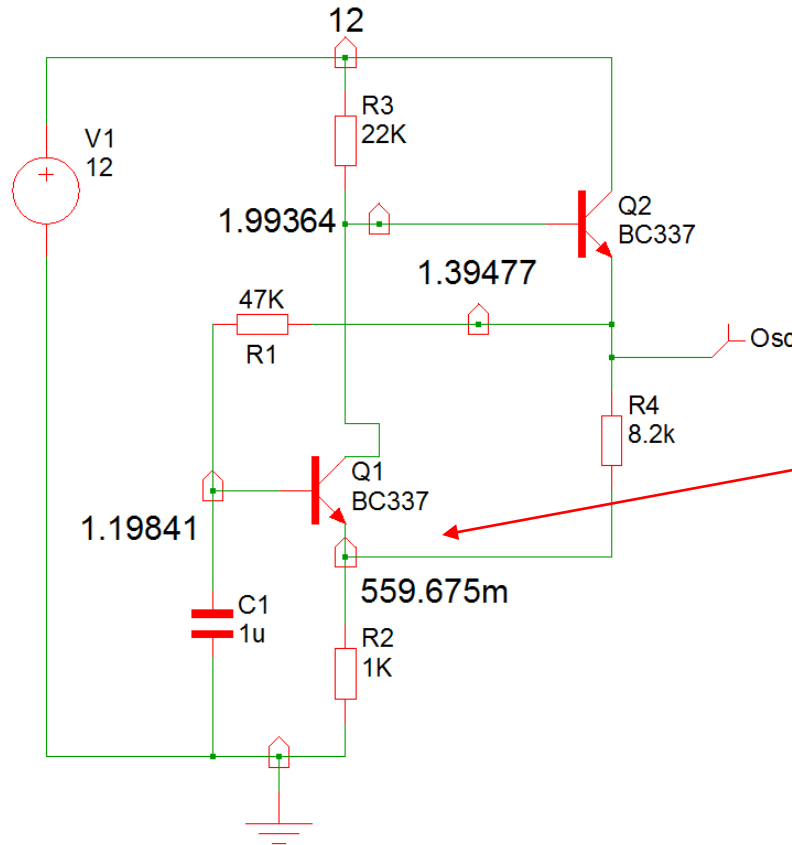

- Most SPICE programs will annotate the bias voltages and currents
  - Invaluable to troubleshooting
- Placing other “probes” allows determination of currents as well



**ARRL** The national association for  
AMATEUR RADIO



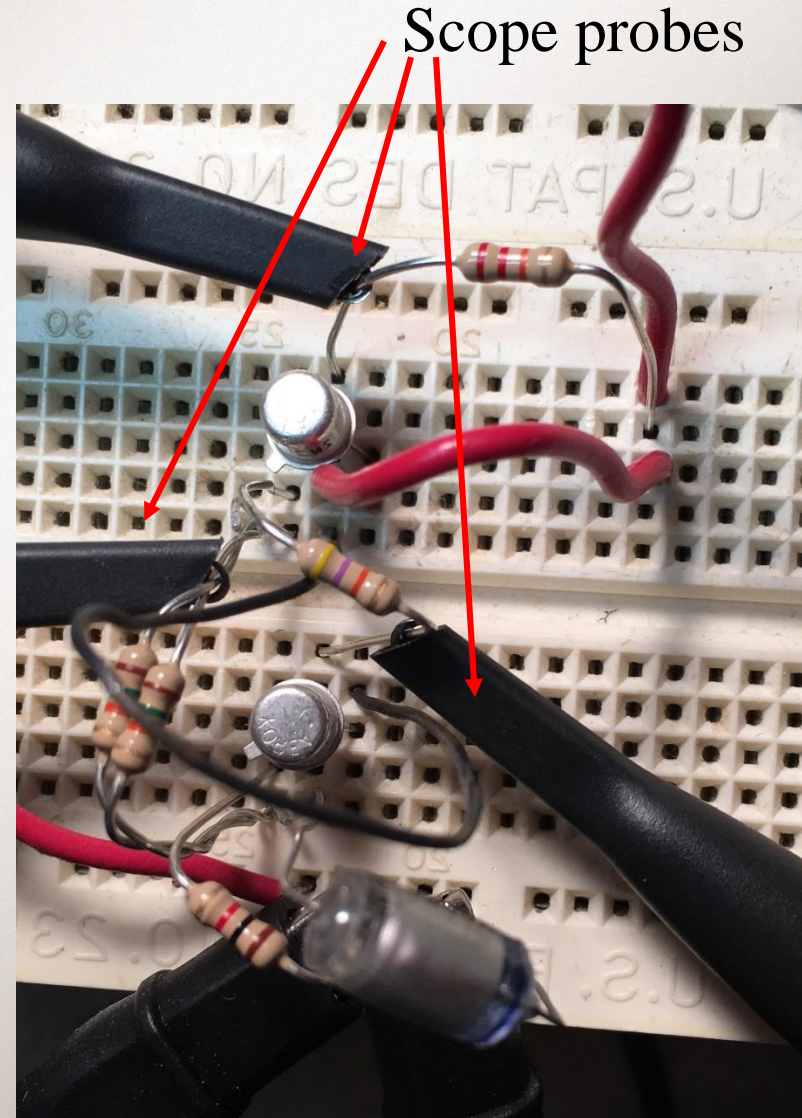
# Actual Breadboard – in 20 minutes



Yellow:  $Q_1$  base  
Blue:  $Q_2$  emitter – Output  
Magenta:  $Q_1$  collector





**ARRL** The national association for  
AMATEUR RADIO








# Advanced Analyses - FFTs

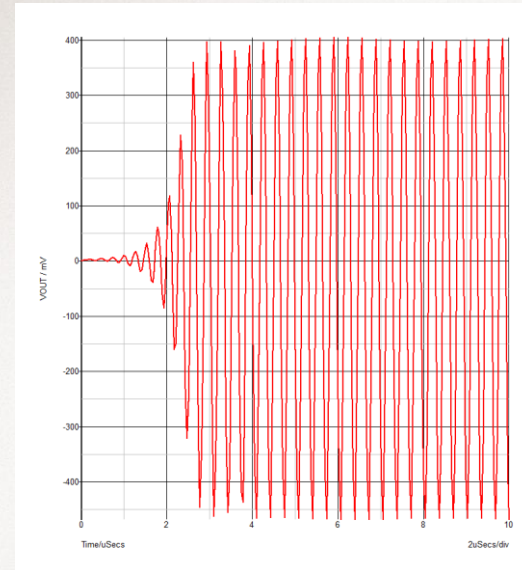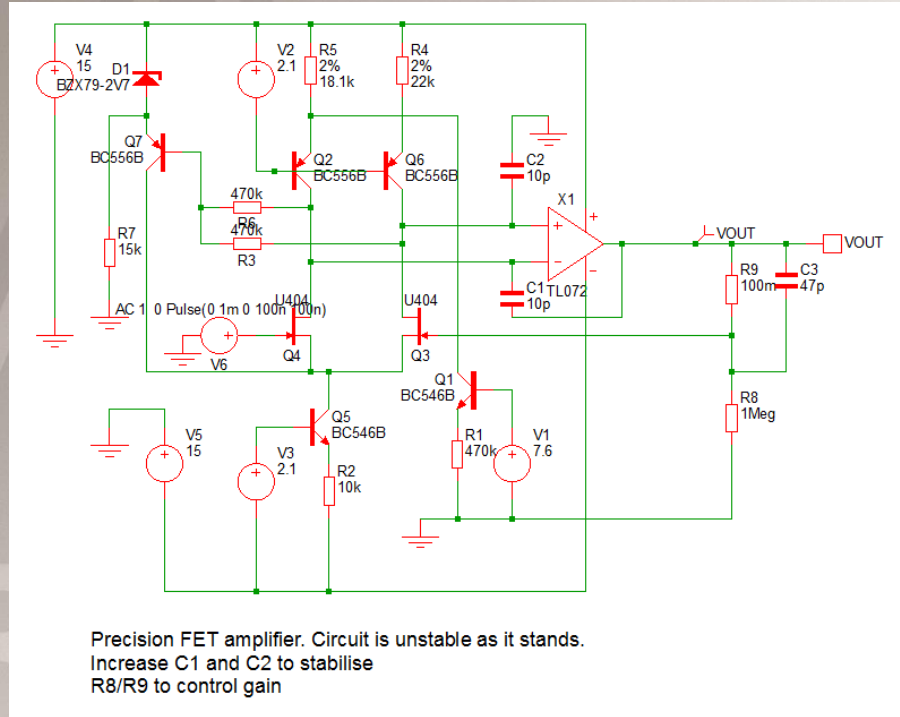

Time  
Domain

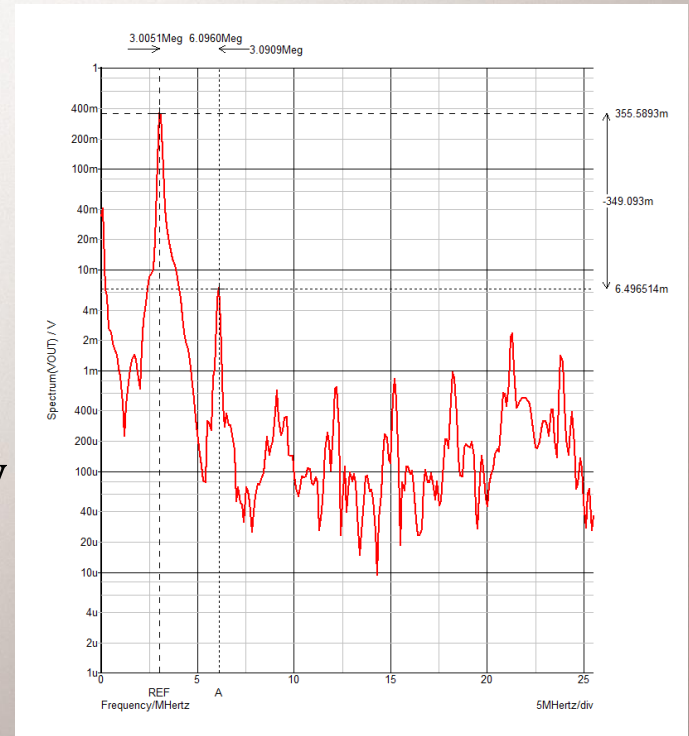

Multi-Stage amplifier with sinewave input

Frequency  
Domain

2<sup>nd</sup> harmonic down 80 dB




**ARRL** The national association for  
AMATEUR RADIO




# Design Sparc for PCB Layout

Lowpass Filter  
for 160m

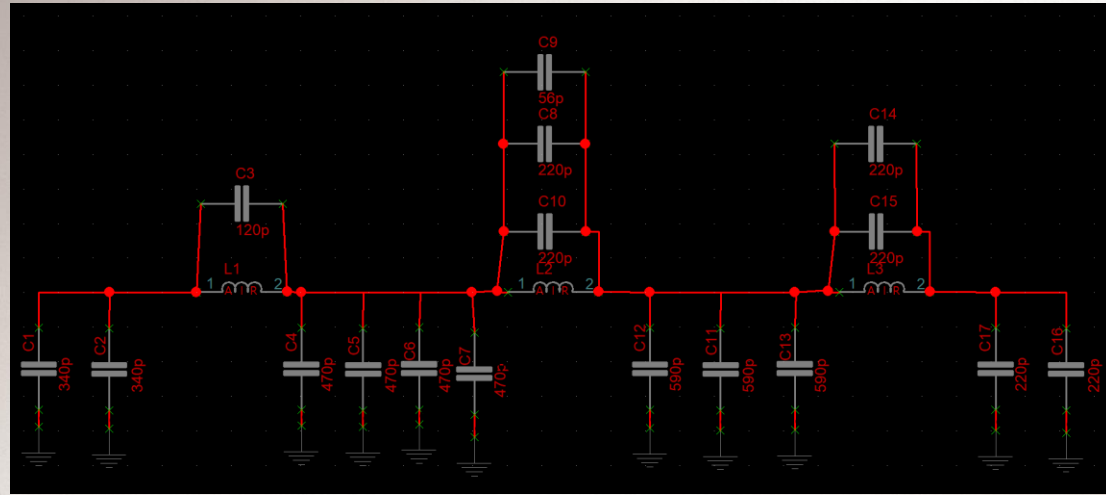

Microstrip Layout  
of Filter

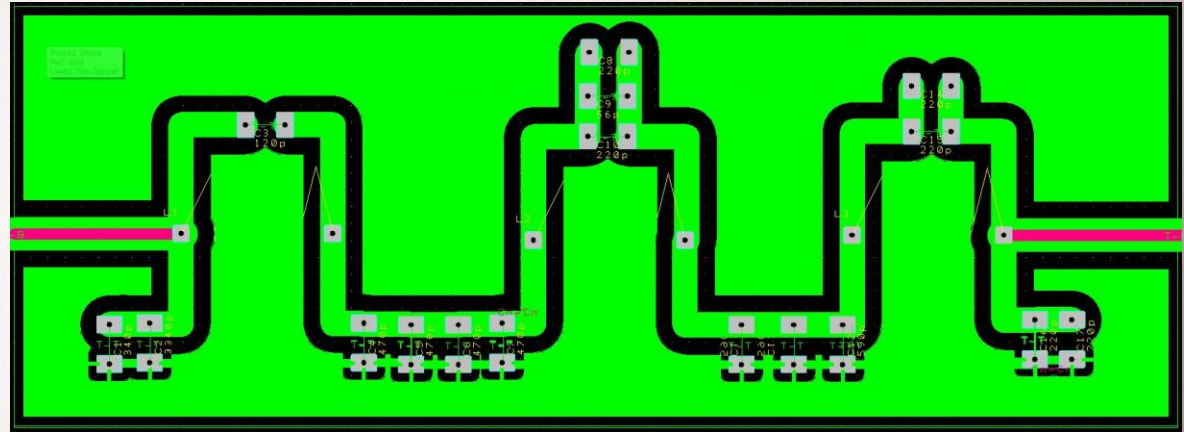

**ARRL** The national association for  
AMATEUR RADIO





# Putting EXCEL to Work

Formulae in ARRL Antenna Handbook allow for tower loading calculations – performed in Excel

**C31XR ONLY - 50 MPH**

Tower Hgt	% Loading
25	25.1
30	29.96
35	34.83
40	39.69
45	44.56
50	49.42
55	54.29
60	59.15
65	64.02
70	68.88
72	70.83

**C31XR & D-240- 50 MPH**


Tower Hgt	% Loading
25	36.72
30	43.29
35	49.87
40	56.44
45	63.02
50	69.59
55	76.16
60	82.74
65	89.31
70	95.89
72	98.52

**C31XR ONLY - 70 MPH**

Tower Hgt	% Loading
25	85.1
30	101.61
35	118.12
40	134.64
45	151.15
50	167.66
55	184.18
60	200.69
65	217.21
70	233.72
72	240.32

**C31XR & D-240- 70 MPH**

Tower Hgt	% Loading
25	125.03
30	147.41
35	169.8
40	192.19
45	214.57
50	236.96
55	259.34
60	281.73
65	304.12
70	326.5
72	335.46

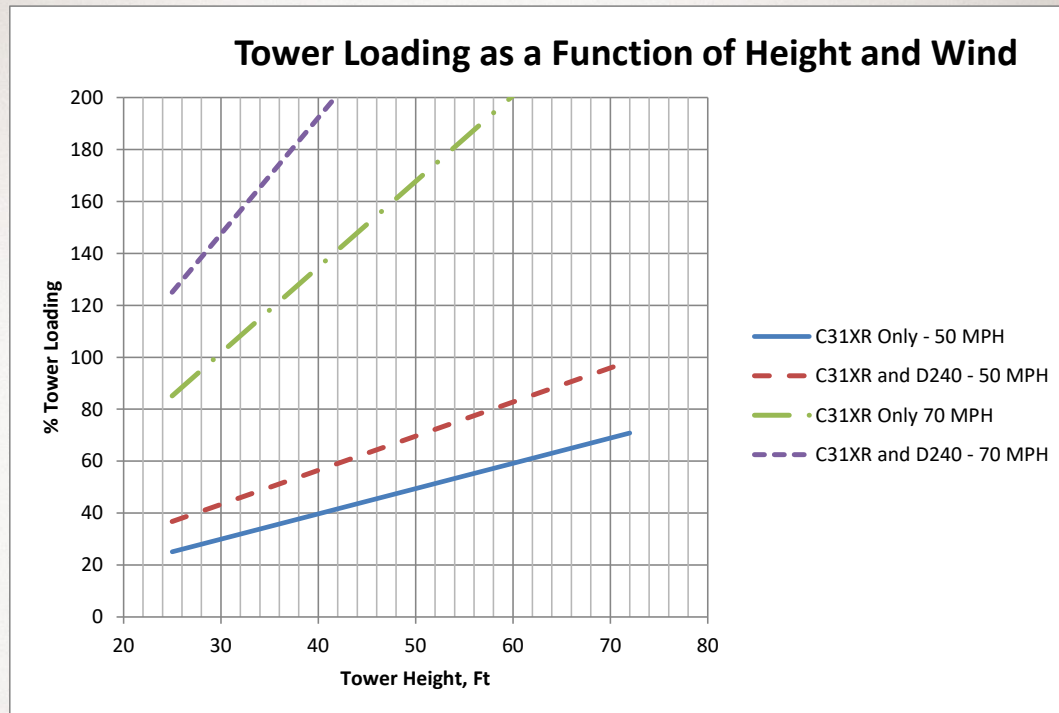

**ARRL** The national association for  
AMATEUR RADIO