



INTERFACING YOUR HF RIG

Jeff Crawford – KØZR



TOPICS COVERED

What is “interfacing” your HF rig mean?

What type of interface is required?

- K3 Specifics
- Relays versus Switching Transistors

Impetus for this discussion

Open-collector Circuit

- How does this work

Implementation for ORION PTT and Receive LNAs

Simple Relay circuit

WHAT IS “INTERFACING” YOUR HF RIG MEAN?

More than a decade ago, the only “interfaces” were:

- Microphone
- Speaker
- Key jack
- ALC
- PTT

All aspects of operation were largely “manual”

- PTT to control T/R of a linear amplifier
- ALC to prevent clipping due to transmitter overdrive
- Frequency was logged “manually”

Today, literally every aspect of HF transceiver operation is available off the back COM or USB port of a HF transceiver

- Microphone line-in for playback of recorded messages
- Audio line-out for recording of audio from RX
- PTT line for computer and keyer control
- COM port commanding of radio

With all this functionality, the amateur must still interface to the station environment

WHAT TYPE OF INTERFACE IS REQUIRED?

- In the general case one must ask, “What type of signal is being handled?”

Some cases are quite straight forward:

- External speaker
- Key paddle
- AUX Receiver input

Others are more complex requiring more investigation

- Key Out
- PTT In
- “Band Outputs” of ACC on K3

- What Options to consider?


If the signal is simply a voltage at some current level:

- A relay could be used
- A switching transistor implementation could be used

If the signal is RF:

- A suitable relay is likely required
- A simple switching transistor is not suitable

Backside of Elecraft K3

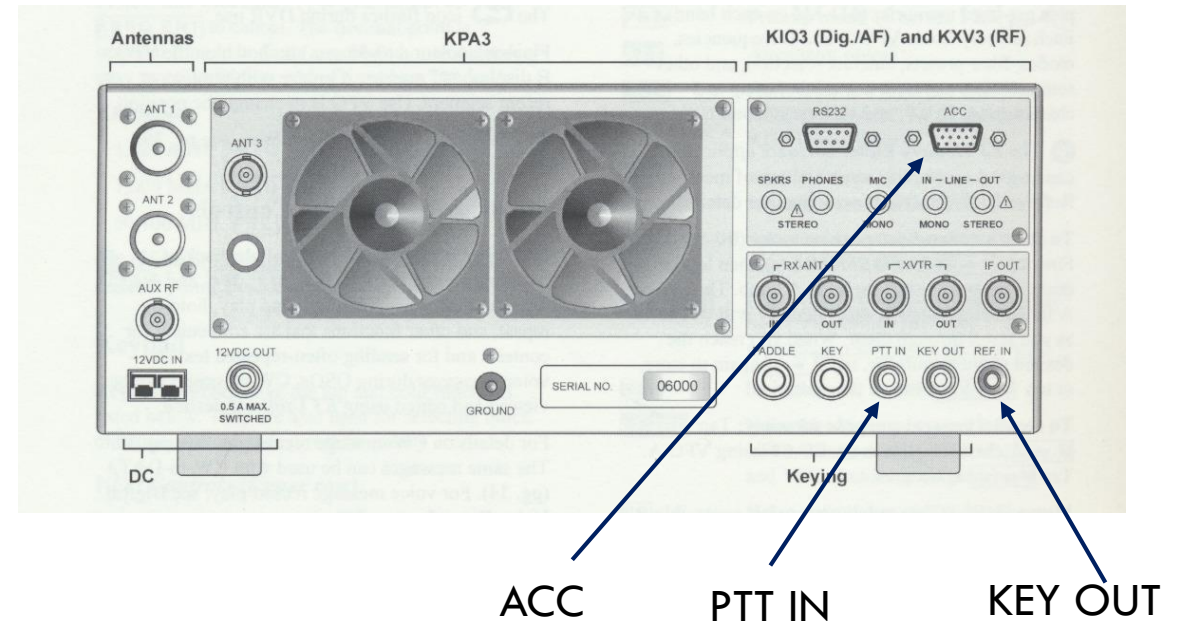



SOME K3 SPECIFICS

PTT IN: Use with a footswitch or other external transmit control device

- PTT IN could be a connection to “ground”
 - From a switching transistor
 - A separate relay
 - An external keyer like “Winkeyer”

KEY OUT: the amplifier T-R relay keying output, capable of keying up to +200 VDC at 5 amps

- A relay internal to the K3 is capable of switching at these levels
 - The higher voltage and current requirement is generally found only in older amplifiers such as Collins, Drake, and Heathkit (if no other modifications have been made)

“Band Outputs” of the ACC connector are TTL levels in most cases: 0 or +5V

- In earlier K3s An external “pull-up” resistor to 5 V may be required
 - The “pull-up” will be discussed shortly

**ACC is accessory connector on K3



WHEN TO USE A MECHANICAL VS TRANSISTOR SWITCH?

You may not have a choice in this

- RF signals need to be switched by a relay suitable for the frequency
 - Switching delays of 10s of milliseconds
 - Reed relays are among the fastest in response time
- Relays require some added circuit attention – to be discussed

- In the case of switching only voltages
 - A transistor switch can respond in 10s of nanoseconds
 - Literally no “wear-out” mechanisms


Terminology associated with a switching transistor, or solid state switch

- The term “Open Collector” is often found
 - In widespread use due to its generality – more to come

IMPETUS FOR THIS DISCUSSION



Station KOZR

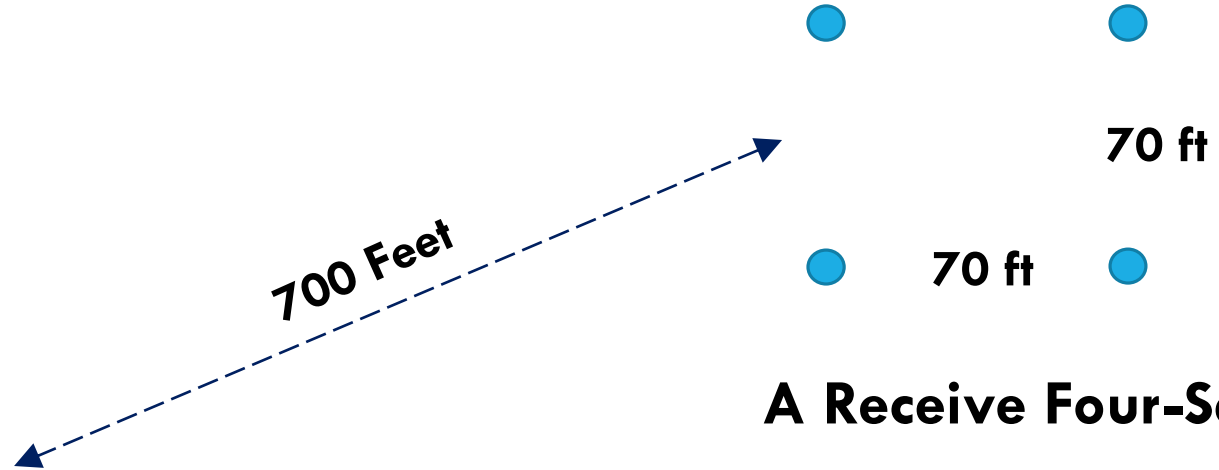

A Receive Four-Square

- Each antenna element is 8 Ft stainless steel “whip”
- Each element has at its base an amplifier that is switched on in “receive” and “off” in transmit



IMPETUS FOR THIS DISCUSSION

Approximately six weeks ago, the switching unit used to activate/deactivate my active receive array used on 160m and 80m failed

- It is an overly complex unit (DX Engineering Time Sequencer) wherein I used a fraction of its capability
- I chose to simplify this with my own array driver circuit


The active array is toggled on/off by PTT signals from my ORION II transceiver

- Consideration of the “Amp Out” line shows an “open-collector” configuration
- In “transmit” the “Amp Out” jack measures ~ 13 VDC
 - In Transmit, “Amp Out” needs to be ~ 0 V
 - An inverter is needed

PTT OUTPUT OF ORION II



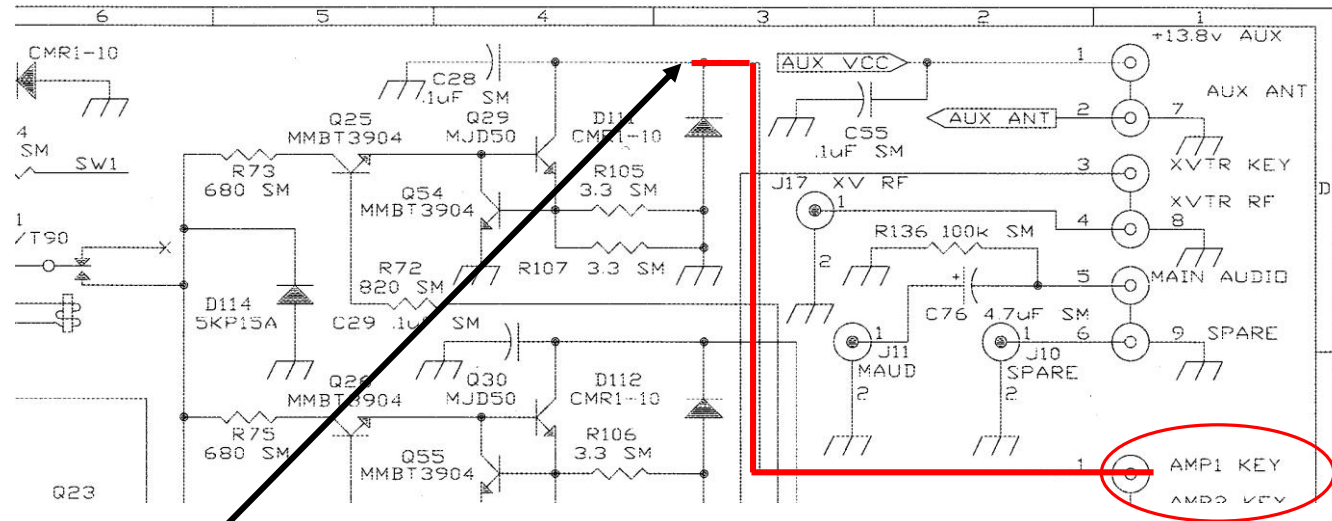Partial schematic of the ORION II transceiver



Other than a diode to protect the MJD50 transistor from a negative voltage, there is no collector voltage per say

Bottom line: No voltage is being applied to the transistor collector until YOU provide a voltage


SOME TRANSISTOR REVIEW



When base-emitter junction forward biased:


- transistor is "On"
- current flows

$$V_{BE} \sim 0.7$$

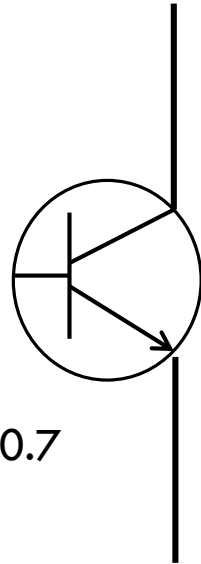

Current flow

$$V_{BE} \sim 0$$

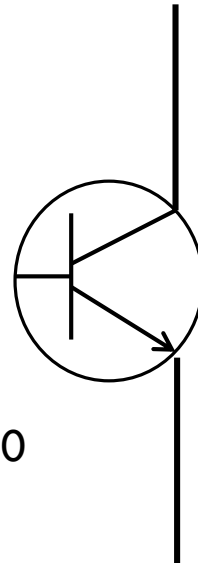


No Current flow

When base-emitter junction not ~ 0.7 V:


- transistor is "Off"
- No current flows

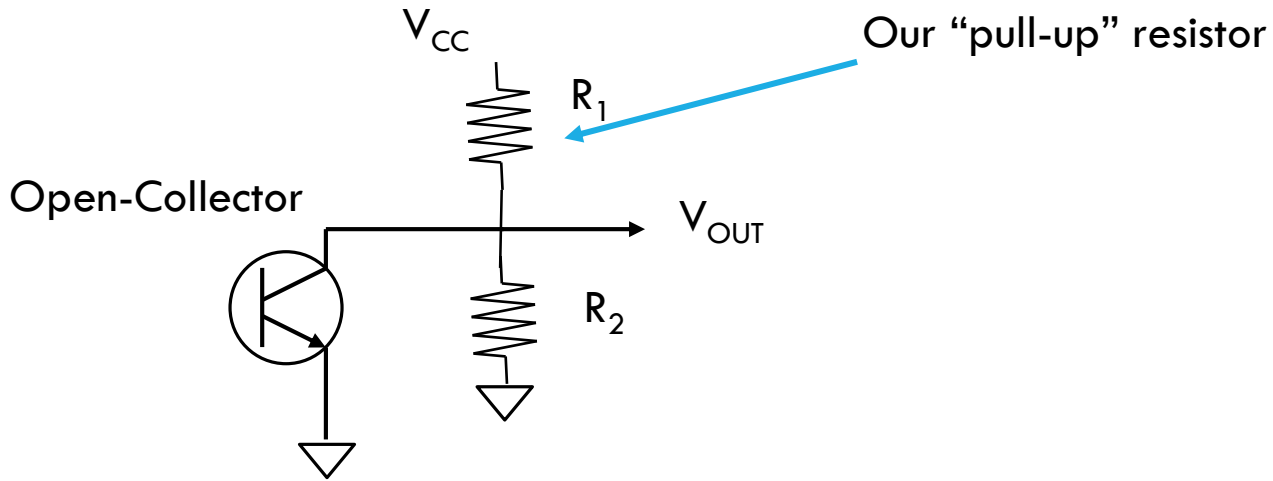SIMPLIFIED VIEW OF THE OPEN COLLECTOR WITH PULL-UP



R_2 actually represents the input impedance of a subsequent transistor as we will see shortly

A SIMPLIFIED VIEW

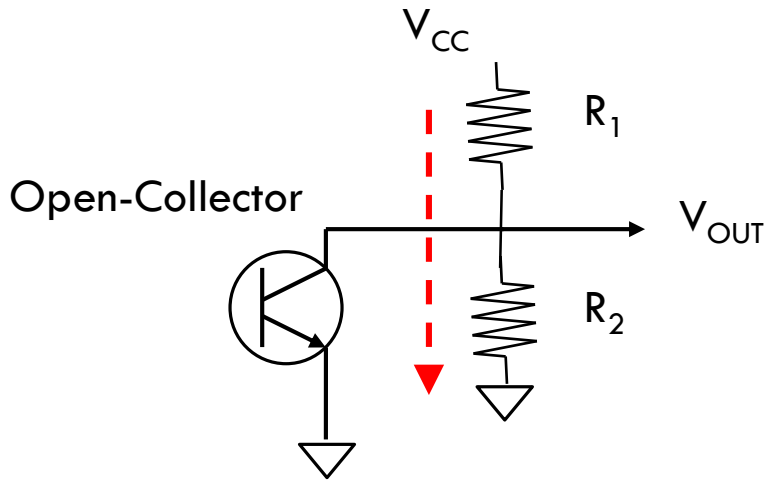

Scenario: NPN transistor is “Off”


- Current flows “only” through R_1 and R_2
with V_{OUT} given by

$$V_{CC} \times R_2 / (R_1 + R_2)$$

- $i_C = i_E \sim 0$




A SIMPLIFIED VIEW

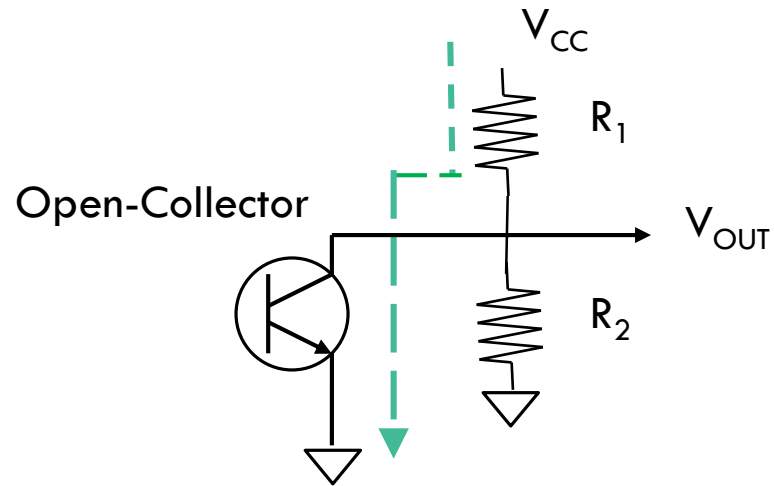

Scenario: NPN transistor is “On”

- Current flows “only” through R_1 and the transistor to ground
- The collector voltage is ~ 0.1 V to 0.2 V which, for most circuits, would be interpreted as “ground” or 0
- V_{OUT} is 0
- i_C determined largely by R_1

A SIMPLIFIED VIEW - REVIEW

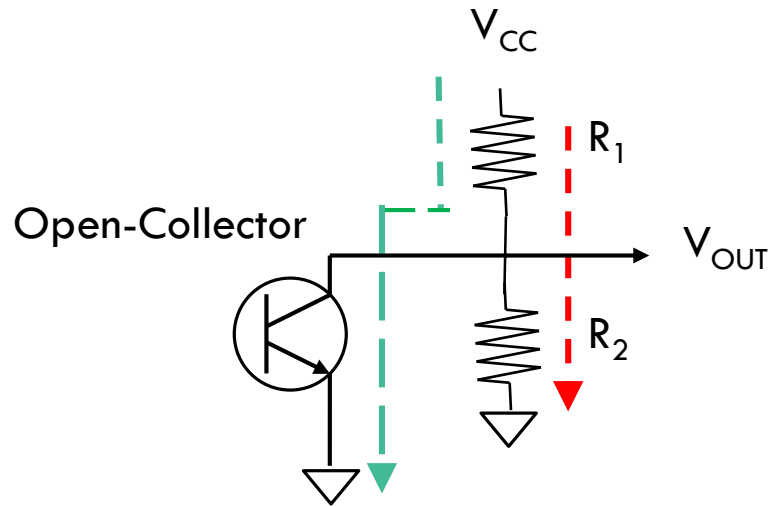

R_1 , which is tied to an “external” V_{CC} , is our “pull-up” resistor.

R_2 actually represents the input impedance of a subsequent transistor as we will see shortly

Scenario: NPN transistor is “Off” (red)

- Current flows “only” through R_1 and R_2 with V_{OUT} given by

$$V_{CC} \times R_2 / (R_1 + R_2)$$


Scenario: NPN transistor is “On” (green)

- Current flows “only” through R_1 and the transistor to ground

- The collector voltage is ~ 0.1 V to 0.2 V which, for most circuits, would be interpreted as “ground” or 0

Guidelines are generally provided in the documentation for the range of R_1 values to use. In the case of my ORION transceiver, the range is 2.2K to 10 K ohms

A SIMPLIFIED VIEW — THE OUTCOME

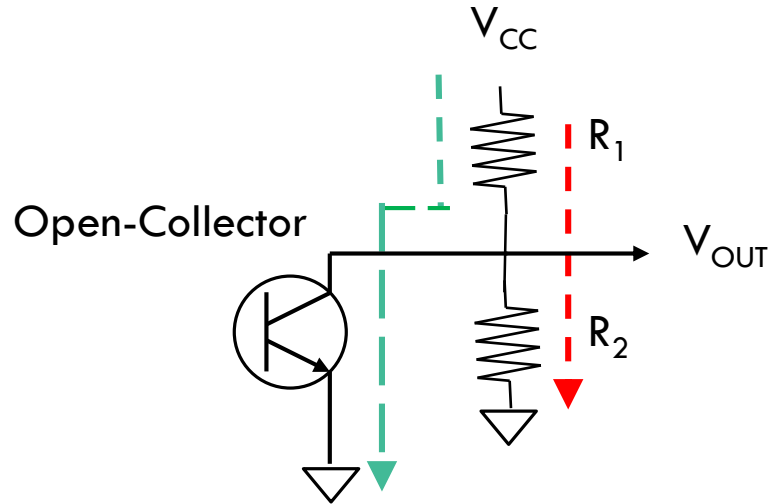

The “universal” applicability of the open-collector is seen when one considers the simple formulas just presented

$$ON : V_{OUT} \approx 0.2V$$

$$OFF : V_{OUT} = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

NPN State

--- On
--- Off

If R_2 large compared to R_1 , most of V_{CC} appears at V_{OUT}


If interfacing to **TTL** circuits, choose $V_{CC} = 5\text{ V}$

If directly driving a relay, choose $V_{CC} = 13.8\text{ V}$

If directly driving **CMOS**, choose $V_{CC} = 3.3\text{ V}$

The open-collector configuration allows you to “tailor-make” the necessary voltage interface levels

ACTUAL IMPLEMENTATION

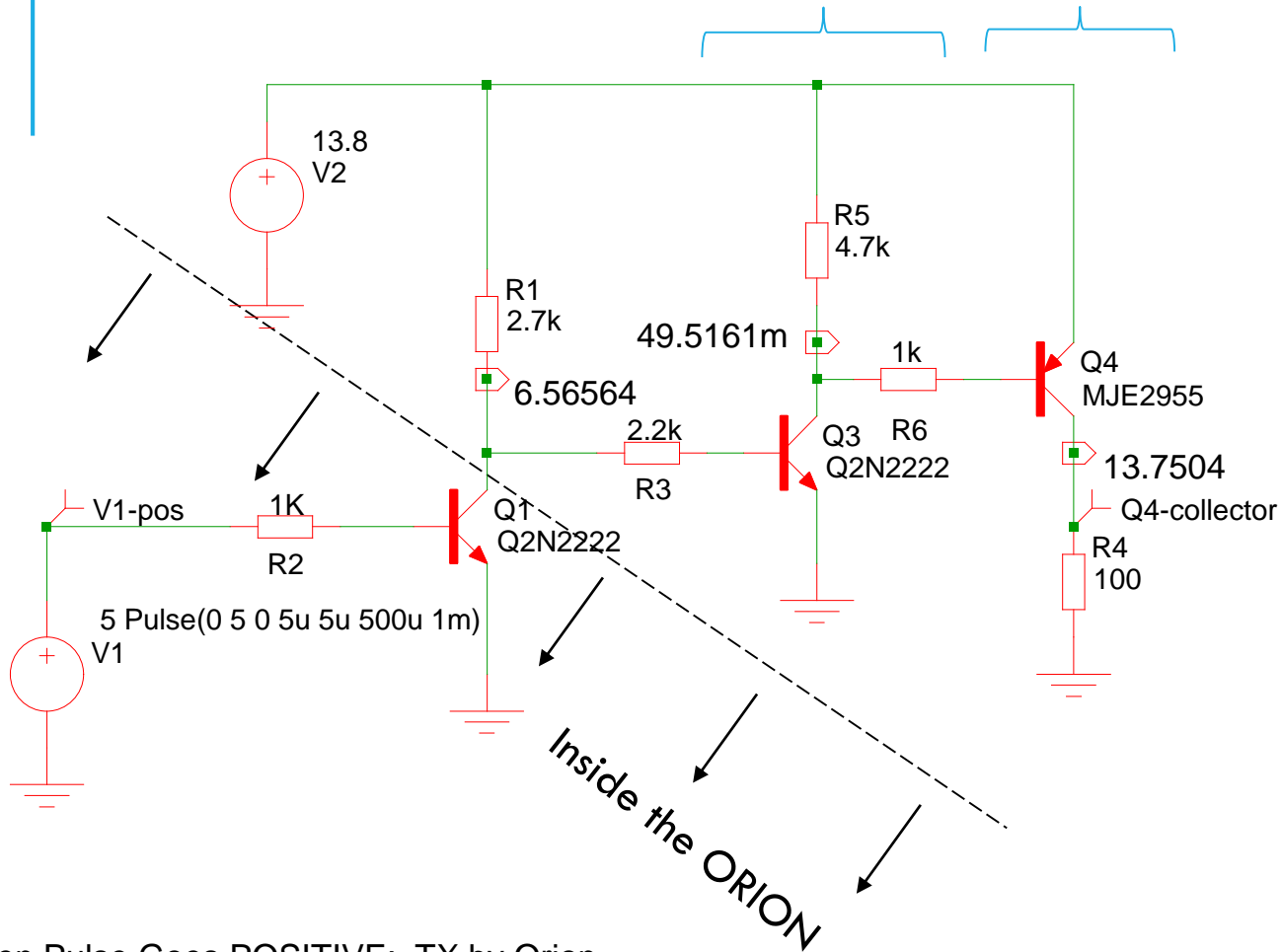

When Pulse Goes POSITIVE: TX by Orion
 When Pulse goes ZERO: RX by Orion

R₃ and R₆ chosen to keep base current to reasonable levels

When the ORION NPN (Q₁) goes high

- Q₁ is turned “on”
- Q₁ collector goes to its “low” state, here ~ 0.1 V (Q₁ almost short-circuit)
- Q₃ base is now “low”, so Q₃ turns “off”
- Q₃ collector current is ~ 0, so base of Q₄ is near 13.8 V --- Q₄ is “off”
- No current flow through Q₄ so no current to R₄, the “load”

When the ORION NPN (Q₁) goes “low”

- Q₁ is turned “off”
- Q₁ collector goes to its “high” state, here ~ 6.6 V
- Q₃ base is now “high”, so Q₃ turns “on”
- At Q₃ collector, voltage is ~ 0.1 V
- Q₄ emitter-base now forward biased so Q₄ turns “on”
- Current flow through Q₄ delivers power to R₄, the “load”




SIMETRIX SIMULATION WAVEFORMS

When ORION transmits, LNAs “off”
so V_{OUT} needs to be low

When ORION receives, want LNAs “on”
so V_{OUT} needs to be high

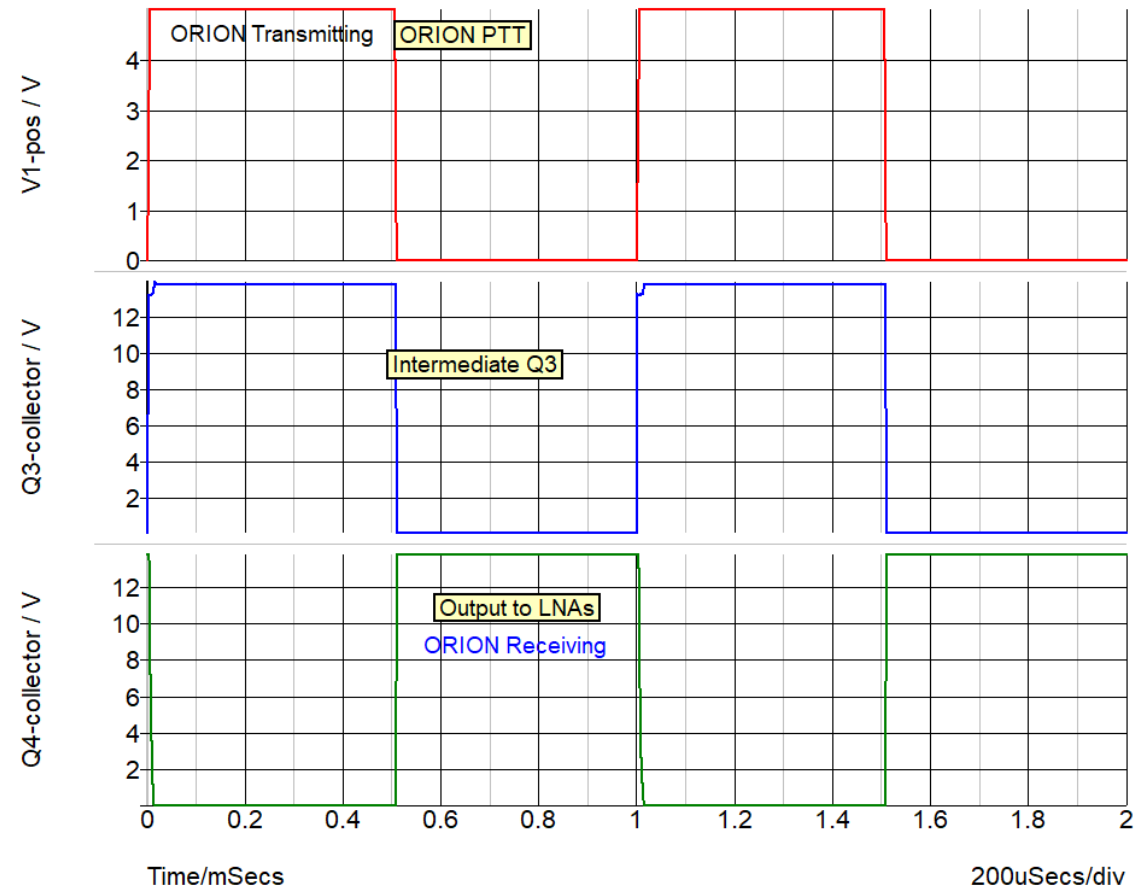As seen, switching is almost “instantaneous”
whereas a relay would have 10’s of
milliseconds delay




Simetrix is a “SPICE” type program, available “free” over the internet with a node limitation of ~ 50

FOUR-SQUARE DRIVER IMPLEMENTED

A 3" x 3 1/2" PCB placed inside the receive array controller does the work

One additional hole for the PTT RCA jack

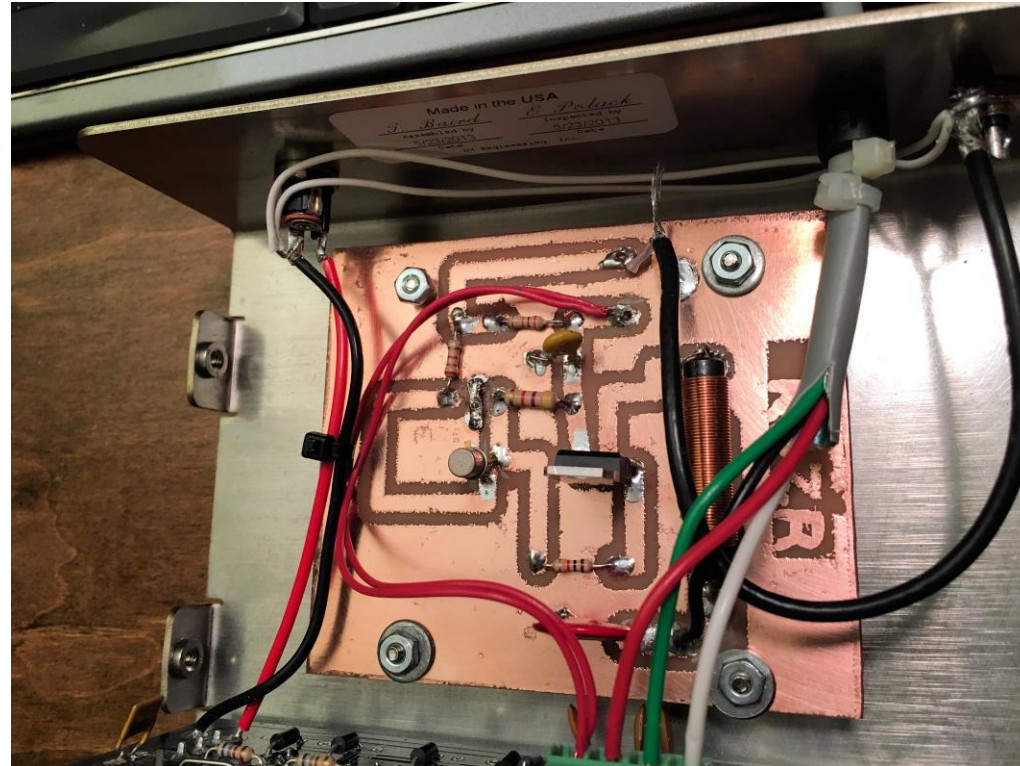If anyone is doing their own PCBs and has some suggestions on improving success with narrow line widths, please talk with me 😊





SUMMARIZING

If no PTT polarity change is needed, add pull-up resistor and one transistor to do the switching

If PTT polarity needs changing, add pull-up resistor, transistor to “invert” the PTT signal, and one transistor to do the switching

Circuits such as this are the easiest to build


Transistor is either “on” or “off”, making resistor selection much simpler

SIMPLE RELAY DRIVER



Situation is simpler if no “inverter” is required for the PTT line

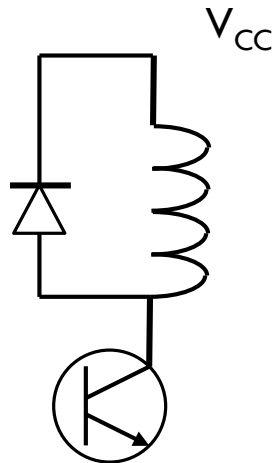Possible to directly drive a small relay using the open-collector output PTT-Out signal



The inductor represents the relay in use

The diode **MUST** be positioned as indicated

Inductors react to sudden transitions in their current

A voltage of the reverse polarity occurs when snapped “off” from an “on” state

If the relay were “on” and ‘instantaneously” switched “off”, a voltage of the opposite polarity occurs according to

$$V_L = L \frac{di}{dt}$$

Example: $L = 200 \mu\text{H}$, $I = 50 \text{ ma}$, $dt = 50 \text{ nsec}$

$$V_L = 200 \times 10^{-6} \times \frac{0.05}{50 \times 10^{-9}} = 200 \text{ V}$$

More than enough reverse voltage to destroy your transistor