

A COMMUNICATIONS RECEIVER

FOR 9 TO 12 MHZ

EE 399


Jeff Crawford

## TABLE OF CONTENTS

The Superheterodyne Receiver—An Overview	(i)
A Communications Receiver for 9 to 12 MHz	(1)
Design With Two-Port Parameters	(1)
The Actual Design	(6)
Mixer	(9)
IF Amplifiers	(12)
Power Supply	(17)
Parts List	(19)
Schematic RF and Audio Sections	(20)
Schematic Colpitts Oscillator	(21)
Program For The HP-41C	(22)
References	(26)
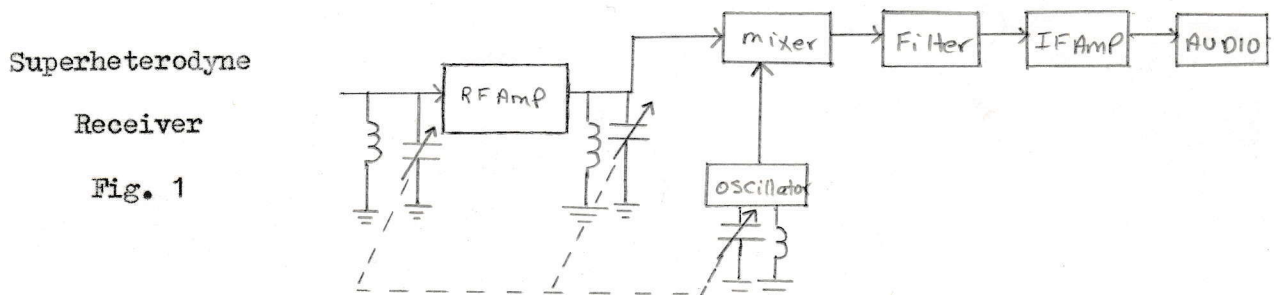
## The Superheterodyne Receiver - An Overview

The superheterodyne receiver is generally considered to be the most appropriate circuit for reception and demodulation of electromagnetic waves containing information. The distinguishing characteristic of this receiver type is that all incoming signals are mixed with the output of a local oscillator and the difference frequency is selected and amplified by intermediate frequency (IF) amplifiers. Excellent performance is obtainable because these amplifiers remain at a fixed frequency and only the RF amplifier and local oscillator need be tunable. Additional stability is inherent in the design due to the fact that the gain is concentrated at two (single conversion) or sometimes three (double conversion) different frequencies.



A block diagram of the receiver is shown above in Fig. 1. The RF amplifier should have a gain of approximately 10 dB in order to establish the overall noise figure of the receiver. Low noise design of this stage is essential because noise generated here propagates throughout the entire receiver. The RF amplifier also serves as a buffer to prevent local oscillator radiation out to the antenna.

The mixer and local oscillator heterodyne the input rf signal from the RF amplifier down to the IF frequency for further amplification. The nonlinearities of the mixer create numerous intermodulation products, one occurring at the IF frequency.

The mixer may be passive (diode mixer) or active (FET or transistor) and provide gain from -10 dB to as high as 30 dB.

The IF amplifier and filter provide the overall bandwidth and adjacent channel selectivity of the receiver. The majority of the receiver's gain is incorporated here, integrated with some form of automatic gain control to provide good dynamic range for all input signal levels. The frequency of the IF amplifiers is usually low (455 kHz to 10.7 MHz) where high signal gain is possible.

The demodulator recovers the information from the IF signal and is of the necessary form for the signal type being received (AM, FM, SSB). This stage may also provide audio-derived AGC to other receiver stages.

Although the superhet receiver offers exceptional performance when compared to a superregenerative or tuned radio frequency receiver, careful design is necessary throughout. The frequency chosen for the IF influences the image rejection of the receiver. Lower IF's provide lower image rejection, higher signal gain and greater selectivity. Higher IF's provide improved image rejection but sacrifice other criteria to be gained at lower IF's. The mixer and RF amplifier stages are the major contributors of noise in the system so each must be of low-noise design to enhance the receivers signal-to-noise ratio. In double conversion receivers, where a second heterodyne mixer is present, noise generated within the mixers is a significant component influencing receiver performance. In its most widespread application as a communications receiver, its advantages outweigh its disadvantages. With the phase-lock loop technology now available, direct conversion receivers are becoming more popular as alternatives to some applications which had in the past employed superheterodyne receivers.

## A COMMUNICATIONS RECEIVER FOR 9 TO 12 MHZ

In an attempt to further my knowledge in my primary area of interest, RF small signal design, this receiver, whose description and development follow, was first conjectured in December, 1981. Considerable effort was made to develop the entire design using the engineering tools I had at that time, as well as investigate other unknown methods which would provide a good engineering approach and a satisfactorily functioning receiver. The most powerful method found applicable to the receiver's design was the use of two-port admittance parameters in the RF small signal design portion of the project.

### DESIGN WITH TWO-PORT PARAMETERS

Design of solid state, small-signal RF amplifiers is a systematic, mathematical procedure with the use of two-port parameters. With this technique an exact solution is available for the complete design problem, the only sources of error being due to parameter variations and strays in the physical circuit. Two-port parameters have the advantage of being applicable to any linear active device and so readily describe the MC1350 integrated circuits used in the IF amplifiers of the receiver.

The major factor in the overall design is the potential stability of the device being used. The stability may be determined by evaluation of the Linville Stability Factor, C, by the use of expression (1).

$$C = \frac{|y_{12}y_{21}|}{2g_{11}g_{22} - \text{Re}(y_{12}y_{21})} \quad (1)$$

When  $C$  is less than one the device is unconditionally stable. When  $C$  is greater than one the device is potentially unstable, the relative stability being dependent upon the source and load connected to the device. The  $C$ -factor is a test for stability under hypothetical worst-case conditions; the input and output open-circuited. If the configuration is potentially unstable, neutralization, unilateralization or the use of restricted source and load values is in order for a stable configuration.

Another stability factor which is used in the development of a relation describing the maximum gain possible with a matched load is the Rollet Stability Factor, (2). Unconditional stability occurs for  $k_r$  greater than one.

$$k_r = \frac{2g_{11}g_{22} - \operatorname{Re}(y_{12}y_{21})}{|y_{12}y_{21}|} \quad (2)$$


The Stern Stability Factor, which finds usage in equations (17) through (24) denotes unconditional stability when  $K$  is greater than one.

$$K = \frac{2(g_{11} + G_s)(g_{22} + G_l)}{|y_{12}y_{21}| + \operatorname{Re}(y_{12}y_{21})} \quad (3)$$

In cases where unilateralization or neutralization are necessary to realize unconditional stability, composite admittance parameters (Fig. 1) may be calculated and used in all relationships to accurately describe the device and feedback network. Network losses, however, are not taken into consideration.

Composite  
Admittance  
Parameters

Fig. 1

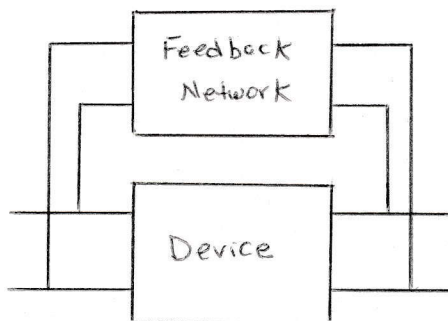

$$\begin{aligned} y_{11c} &= y_{11d} + y_{11f} \\ y_{12c} &= y_{12d} + y_{12f} \\ y_{21c} &= y_{21d} + y_{21f} \\ y_{22c} &= y_{22d} + y_{22f} \end{aligned}$$

A general expression for power gain is

$$G = \frac{|y_{21}|^2 \operatorname{Re}(Y_L)}{Y_L + y_{22} \operatorname{Re}\left(y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L}\right)} \quad (4)$$

Equation (4) does not include any effect due to  $Y_s$ , the source admittance.

A more complete relationship which includes the effects of the degree of input and output matching is the equation for transducer gain, (5).

$$G_t = \frac{4 \operatorname{Re}(Y_s) \operatorname{Re}(Y_L) |y_{21}|^2}{\left| (y_{11} + Y_s)(y_{22} + Y_L) - y_{12}y_{21} \right|^2} \quad (5)$$

The maximum available gain is the theoretical power gain of a linear device with its reverse transfer admittance  $y_{12}$  set equal to zero and its source and load admittances conjugately matched to  $y_{11}$  and  $y_{22}$  respectively.

$$\text{MAG} = \frac{|y_{21}|^2}{4 \operatorname{Re}(y_{11}) \operatorname{Re}(y_{22})} \quad (6)$$

The maximum gain possible by choosing only  $Y_L$  optimally is given by (7) where  $kr$  is the Rollet Stability Factor of (2).

$$G_{\max} = \left| \frac{y_{21}}{y_{12}} \right| \left[ kr - \sqrt{(kr)^2 - 1} \right] \quad (7)$$

Expressions for the input and output admittance of a linear device are described by (8) and (9).

$$Y_{\text{in}} = y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L} \quad (8)$$

$$Y_{\text{out}} = y_{22} - \frac{y_{12}y_{21}}{y_{11} + Y_s} \quad (9)$$

If the maximum possible power gain without feedback is desired for an amplifier, the following relationships determine the source and load admittances required to achieve maximum transducer gain.

$$G_s = \frac{1}{2 \operatorname{Re}(y_{22})} \left[ \left[ 2 \operatorname{Re}(y_{11}) \operatorname{Re}(y_{22}) - \operatorname{Re}(y_{12} y_{21}) \right]^2 - |y_{12} y_{21}|^2 \right]^{\frac{1}{2}} \quad (10)$$

$$B_s = -\operatorname{Im}(y_{11}) + \frac{\operatorname{Im}(y_{21} y_{12})}{2 \operatorname{Re}(y_{22})} \quad (11)$$

$$G_l = \frac{1}{2 \operatorname{Re}(y_{11})} \left[ \left[ 2 \operatorname{Re}(y_{11}) \operatorname{Re}(y_{22}) - \operatorname{Re}(y_{12} y_{21}) \right]^2 - |y_{12} y_{21}|^2 \right]^{\frac{1}{2}} \quad (12)$$

$$B_l = -\operatorname{Im}(y_{22}) + \frac{\operatorname{Im}(y_{21} y_{12})}{2 \operatorname{Re}(y_{11})} \quad (13)$$

The case of potential instability may be handled, as pointed out earlier, by employing an external feedback network to achieve a composite  $y_{12}$  of zero. The necessary design equations for the unilateralized case are derived by first evaluating the composite  $y$  parameters for the linear device and feedback network combination. Making the proper substitutions give equations (14), (15), and (16).

A general expression for unilateralized power gain is

$$G_{pu} = \frac{|y_{21} - y_{12}|^2 \operatorname{Re}(Y_l)}{|Y_l + y_{22} + y_{12}|^2 \operatorname{Re}(y_{11})} \quad (14)$$

The unilateralized power gain with  $Y_l$  conjugately matched to  $Y_{out}$  is given by

$$G_u = \frac{|y_{21} - y_{12}|^2}{4 \operatorname{Re}(y_{11} + y_{12}) \operatorname{Re}(y_{22} + y_{12})} \quad (15)$$



Unilateralized transducer gain is given by

$$G_{tu} = \frac{4 \operatorname{Re}(Y_s) \operatorname{Re}(Y_L) |y_{21} - y_{12}|^2}{|(y_{11} + y_{12} + Y_s)(y_{22} + y_{12} + Y_L)|^2} \quad (16)$$

Equations (1) through (16) were all that were necessary in the receiver design due to the unconditional stability of the configuration used. In the case of potential instability, equations for computing the conductance and susceptance of both  $Y_s$  and  $Y_L$  for maximum power gain and a particular Stern Stability Factor,  $k$ , are listed below.

$$G_s = \sqrt{\frac{k \left[ |y_{12} y_{21}| + \operatorname{Re}(y_{12} y_{21}) \right]}{2}} \cdot \sqrt{\frac{\epsilon_{11}}{\epsilon_{22}}} - \epsilon_{11} \quad (17)$$

$$G_L = \sqrt{\frac{k \left[ |y_{12} y_{21}| + \operatorname{Re}(y_{12} y_{21}) \right]}{2}} \cdot \sqrt{\frac{\epsilon_{22}}{\epsilon_{11}}} - \epsilon_{22} \quad (18)$$

$$B_s = \frac{(G_s + \epsilon_{11}) Z_o}{\sqrt{k \left[ |y_{12} y_{21}| + \operatorname{Re}(y_{12} y_{21}) \right]}} - b_{11} \quad (19)$$

$$B_L = \frac{(G_L + \epsilon_{22}) Z_o}{\sqrt{k \left[ |y_{12} y_{21}| + \operatorname{Re}(y_{12} y_{21}) \right]}} - b_{22} \quad (20)$$

$Z_o$  is the real value of  $Z$  which results in the smallest minimum of the following relationship.

$$Z^3 + [k(L + M) + 2M] Z - 2N \sqrt{k(L + M)} = 0 \quad (21)$$

$$Z = \frac{(B_s + b_{11})(G_L + \epsilon_{22}) + (B_L + b_{22})k(L + M)/2(G_L + \epsilon_{22})}{\sqrt{k(L + M)}} \quad (22)$$

$$L = y_{12} y_{21}$$

$$M = \operatorname{Re}(y_{12} y_{21})$$

One other alternative available to the designer to obtain a stable configuration involves mismatching  $G_s$  to  $g_{11}$  and  $G_l$  to  $g_{22}$  by an equal ratio. If a mismatch ratio,  $R$ , is defined as

$$R = \frac{G_l}{g_{22}} = \frac{G_s}{g_{11}} \quad (25)$$

then  $R$  may be computed for any particular circuit stability factor using the equation

$$(1 + R)^2 = k \left[ \frac{|y_{21}y_{12}| + \text{Re}(y_{12}y_{21})}{2g_{11}g_{22}} \right] \quad (26)$$

The power of these mathematical equations is the alternative use of hybrid, impedance, or scattering parameters and the appropriate conversion equations between parameter types. A correct mathematical design approach is made available from very low frequencies through the microwave range.


A program suitable for the HP-41C calculator was written for all relationships thus far developed exclusive of (17) through (24). Extensive use of this program was used to develop the receiver design. The program is included at the end of this paper.

#### THE ACTUAL DESIGN

A series-tuned Colpitts oscillator with two intermediate stages of buffering is used in the receiver as the local oscillator. Two JFETs, MPF102, and a 2N2222A transistor are used in the configuration with diode switching in the tank circuit for multiple band coverage.

Colpitts Oscillator with  
Diode Switching

Fig. 2

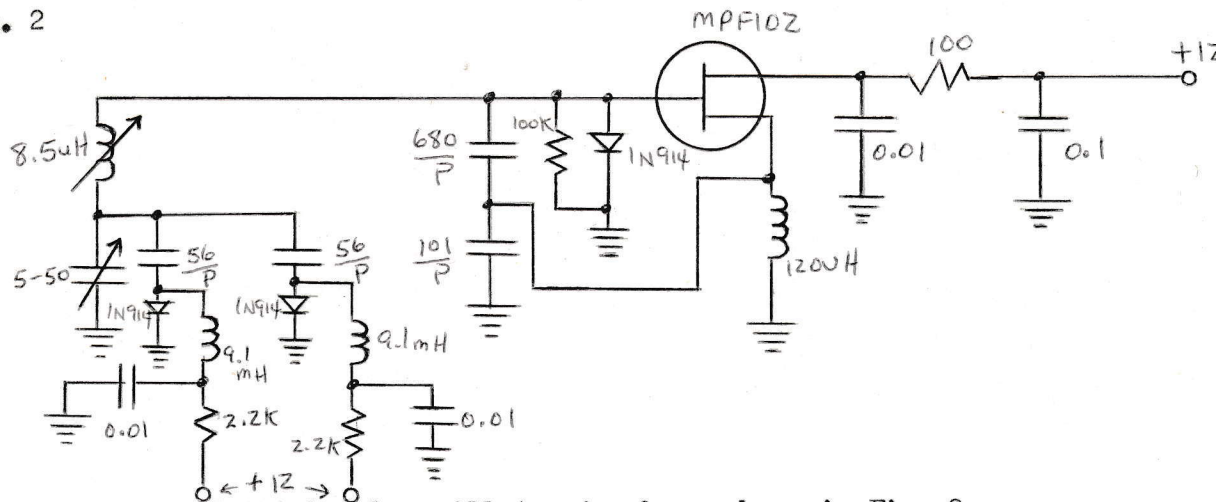

The main portion of the local oscillator is shown above in Fig. 2.

The equation describing the frequency of operation of the oscillator tank is

$$\omega_0 = \sqrt{\frac{1}{L} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)}$$

$C_1$  = Total capacitance in series with the inductor

$C_2$  = Total capacitance of capacitive feedback network

The 9.1 mH chokes in the tank serve to decouple the switching voltage applied to the 1N914 diodes in the tank circuit. The 680 pF and 101 pF capacitors affect the frequency of operation and also establish the proper amount of feedback for stable operation. The source follower has decoupling on its drain in the form of 0.01 and 0.1 uF capacitors and 100 ohm resistor to prevent rf from entering the power supply. Output is developed across the 120 uH inductor and capacitively coupled to a second source follower which provides a light load for the oscillator (see Fig. 9). The 2N2222A in a common emitter configuration develops the output signal which is applied to the local oscillator input of the MC1596G mixer.

The first stage encountered by a received signal is a three-section Chebycheff bandpass filter with a passband of 8 to 12 MHz.



The MC1596G is an excellent device for use as a balanced modulator or demodulator and provides high common mode rejection in addition to adjustable gain. The output collectors of the device are cross coupled so that full wave balanced multiplication of the two input signals occurs. The direct result is an output spectrum consisting only of the sum and difference of the two input frequencies. The approximate voltage gain for the MC1596 in low-level ac applications is

$$\text{Voltage Gain} = \frac{R_L V_c (\text{rms})}{2 \sqrt{2} \frac{kT}{q} (R_E + 2r_e)} \quad (28)$$

$R_E$  = resistance between pins 2 and three

$r_e = 26 \text{ mv}/I_E$  (ma)

$kT/q = 26 \text{ mv}$  at room temperature

The use of (28) gives a voltage gain of 5 dB for a 50 microvolt input signal.

The input admittance of the MC1596 is extremely invariant in the frequency range of interest (Table 1) so no form of matching is necessary. The input capacitance is so low that no attempt is made to cancel it with an equal amount of inductive reactance.

Input Characteristics	Frequency	Input Impedance	
Table 1	5 MHz	240 K ohms	2.05 pF
	10 MHz	1 Meg ohm	2.05 pF
	15 MHz	240 K ohms	2.05 pF


The necessary biasing for the MC1596 is derived from information provided by an application note on the MC1596 and MC1496 by Motorola. The output of the mixer remains at 455 kHz and must be matched to the next 3000 ohm stage, the 455 kHz filter, for maximum signal transfer.

Several widely used impedance matching configurations and their corresponding equations are shown below.

$$(29A) \quad R_1 > R_2$$

$$X_L = \sqrt{R_1 R_2 - R_2^2}$$


$$X_C = \frac{R_1 R_2}{X_L}$$

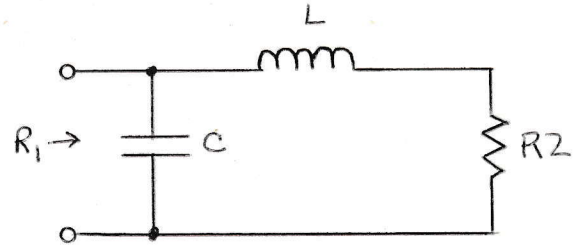

$$(29B) \quad R_2 > R_1$$

$$X_L = R_2 \sqrt{\frac{R_1}{R_2 - R_1}}$$


$$X_C = \frac{R_1 R_2}{X_L}$$

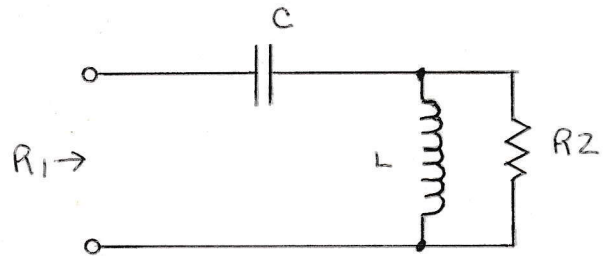

$$(29C) \quad R_1 < R_2, \quad N > \sqrt{R_2/R_1 - 1}$$


$$X_L = R_2 / N$$
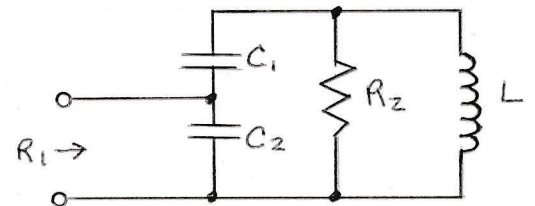
$$X_{C2} = \frac{R_1}{\sqrt{\frac{R_1(N^2 + 1)}{R_2} - 1}}$$




$$X_{C1} = \frac{R_2 N}{N^2 + 1} \left( 1 - \frac{R_1}{N X_{C2}} \right)$$

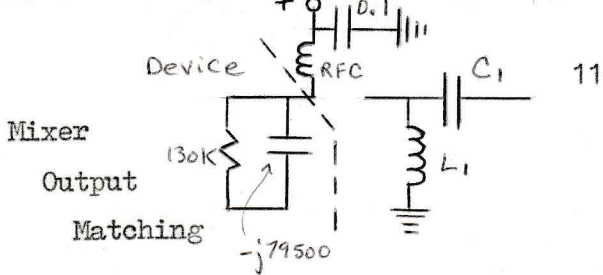The matching scheme of (29B) is used to match the output of the mixer because it conveniently allows use of one inductor for both power line isolation and impedance matching.



Match 130 K ohms to  
3 K ohms

Fig. 5

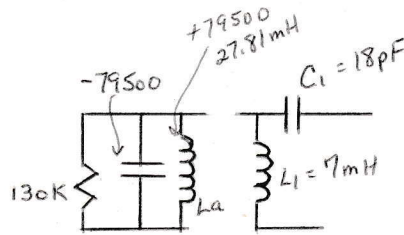

$L_a$  cancels output  
capacitive reactance

$$X_{L1} = 130 \text{ K} \sqrt{\frac{3 \text{ K}}{130 \text{ K} - 3 \text{ K}}} = 19,980 \text{ ohms}$$

$$X_{La} = 79,500 \text{ ohms}$$

$$L_1 = 7 \text{ mH.}$$

$$L_a = 27.81 \text{ mH}$$


$$X_C = R_1 R_2 / X_L = 19520 \text{ ohms}$$

$$C_1 = 18 \text{ pF}$$

Combining the two inductors yields

$$\frac{(27.81)(7)}{27.81 + 7} = 5.6 \text{ mH}$$

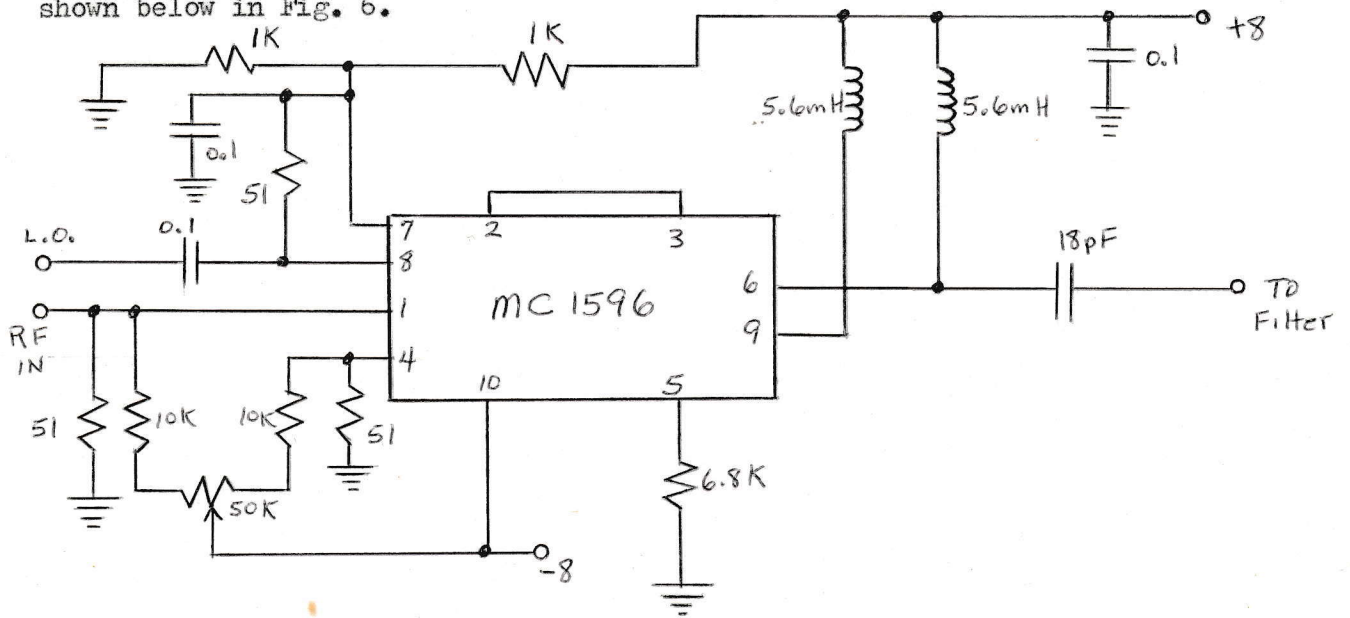The mixer stage with its associated biasing and input-output matching is shown below in Fig. 6.



Mixer

Fig. 6

The IF amplifier consists of two Motorola MC1350 integrated circuits in cascade with an automatic gain control signal applied from a CA3160 differential amplifier. The MC1350 has nearly constant input and output admittances over its entire AGC range and has a very low reverse transfer admittance. Admittance values for the device at 455 kHz are listed in Table 2. The reverse transfer admittance,  $g_{12}$ , is not known exactly, but it does not significantly affect the gain of the device and has only a minimal effect on  $b_{11}$ , the input susceptance.

Admittance Parameters for  
MC1350 at 455 kHz

Table 2

$g_{11}$	0.31	mmhos
$b_{11}$	0.022	mmhos
$g_{12}$	$1(10^{-9})$	mmhos
$b_{12}$	0	
$g_{21}$	0.1594	mmhos
$b_{21}$	-0.01394	mmhos
$g_{22}$	$4(10^{-6})$	mmhos
$b_{22}$	$3(10^{-6})$	mmhos

00031078 (4.0523)

00016001 (-4.997969)

$5 \times 10^{-9}$  (36.87)

Using the admittance values in Table 2 and the appropriate mathematical equations already developed, the following operational characteristics are obtained.

Equation

Data

- (2) Unconditional Stability
- (2) Rollet Stability 14.504
- (7)  $G_{max}$  67.42 dB
- (3) Stern Stability Factor 29.03

(10), (11),  
(12), (13)

Optimum source and load to achieve maximum power gain

$$Y_s = 2.894 (10^{-4}) - j 2.374 (10^{-5}) \text{ mhos}$$

$$Y_L = 3.734 (10^{-6}) - j 3.0225 (10^{-6}) \text{ mhos}$$

The optimum source and load in parallel equivalents are

$$Z_s = 3432 + j 282 \text{ ohms}$$

$$Z_L = 161.8 \text{ K} + j 131 \text{ K ohms}$$

37.4218dB



Coupling from the 455 kHz crystal filter to the input of the first MC1350 is provided by a series 0.05 uF capacitor. No attempt of matching is made because the small mismatch present contributes theoretically to a degradation in gain of only 0.05 dB (5). The output of the first IF stage is transformer coupled by a primary-tuned toroidal circuit to the second stage input. Proper resonance at 455 kHz is provided by an adjustable trimmer capacitor in parallel with the primary. A toroid with a tapped primary is used to provide a load of 30 K ohms for the first stage and also allows dc operating voltages to be applied to the MC1350.

Earlier it was determined that the optimum load for the first stage is  $161.8 \text{ K} + j 131 \text{ K ohms}$ . A simple calculation shows that only 3 pF of stray capacitance has nearly 120 K ohms of reactance so, in order to maintain good stability, a lower value of load impedance is required. Use of (5) shows that with a load of 30 K ohms and the  $Y_s$  previously defined, gain is 63 dB which is more than adequate. The small amount of loss introduced by this mismatch will be very much worth the added stability gained by the lower load impedance.

The actual design of the RF section began with the second IF (progressing toward mixer) and a  $Z_L$  for the second stage of 10 K ohms was chosen. Using equations (5) and (8) gives the optimum source for the second IF stage which is

$$Y_{in} = 3.0847 (10^{-4}) + j 2.2178 (10^{-5}) \text{ mhos}$$

or

$$Z_{in} = 3225 - j 232 \text{ ohms}$$

Returning to the IF transformer calculation,

$$\frac{N_p}{N_s} = \sqrt{\frac{Z_p}{Z_s}} \quad (30)$$

$N_p$  = primary turns

$Z_p$  = primary impedance

$N_s$  = secondary turns

$Z_s$  = secondary impedance

$$\sqrt{\frac{30,000}{3225}} = \text{Turns Ratio} = 3.05$$

A primary inductance of 120 uH is used and data provided by Amidon Associates with the toroid allows proper determination of primary and secondary turns.

A 15 - mix, T - 68 toroid is used. This material has a permeability  $\mu = 25$  and a usable frequency range of 0.1 - 2.0 MHz.  $A_L$  (uH/ 100 turns) for this core size is 180 uH.

$$\# \text{ turns} = 100 \sqrt{\text{desired } L \text{ (uH)} / A_L \text{ value (uH)}}$$


$$\text{Primary} = 100 \sqrt{120/180} = 81.65 \text{ turns}$$

$$\text{Secondary} = 81.65/3 = 27.22 \text{ turns}$$

First IF Stage

Fig. 7

Gain 63 dB

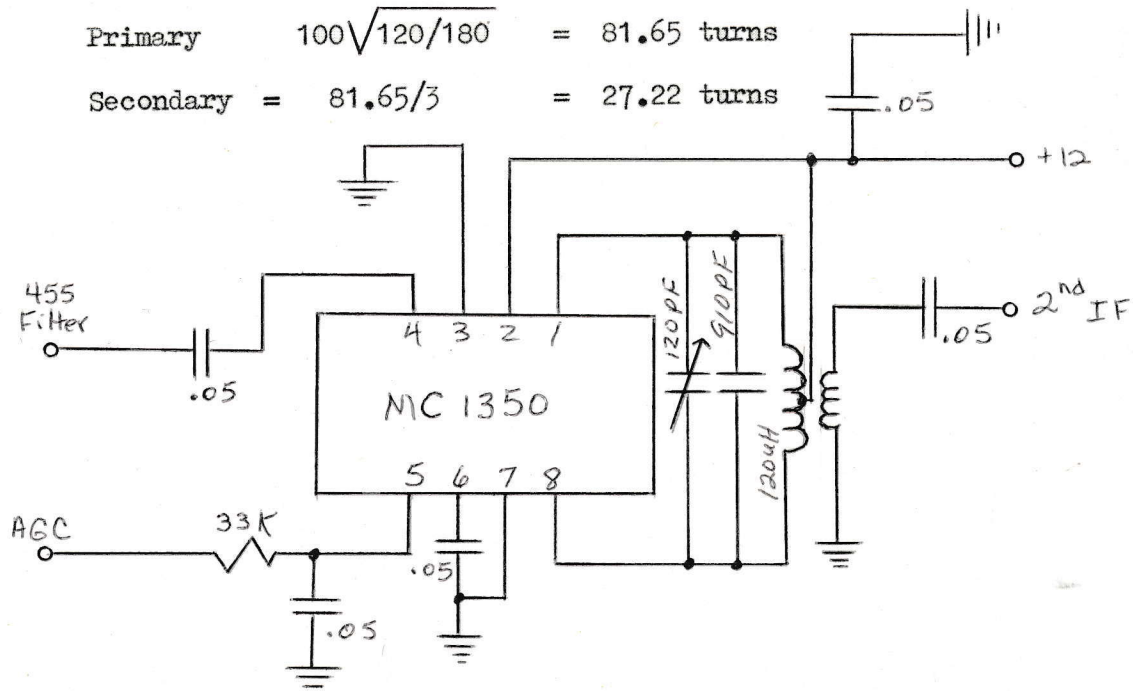


The second stage IF amplifier is designed with the same procedure as just outlined. Once again, no attempt is necessary to match the input of the second stage ( $3225 -j232$  ohms) to the transformer secondary which is very close necessary value. A  $0.05 \mu\text{F}$  coupling capacitor is used to isolate the input from dc ground.

The output of the second IF uses the matching arrangement of (29C). The second IF stage delivers its output to a voltage doubler where the AM signal is demodulated. A  $Z_{in}$  for the voltage doubler of 125 ohms is chosen and a load of 10 K ohms for the output of the second MC1350 is used. With  $Z_{in} = 3225$  ohms and  $Z_{out} = 10 \text{ K ohms}$  for the MC1350, the transducer gain is 58.85 dB (5). Several dB of additional gain could be achieved with a higher  $Z_{out}$  for the stage but this requires a higher than desired Q for the output matching circuit.

Second IF Stage

Fig. 8

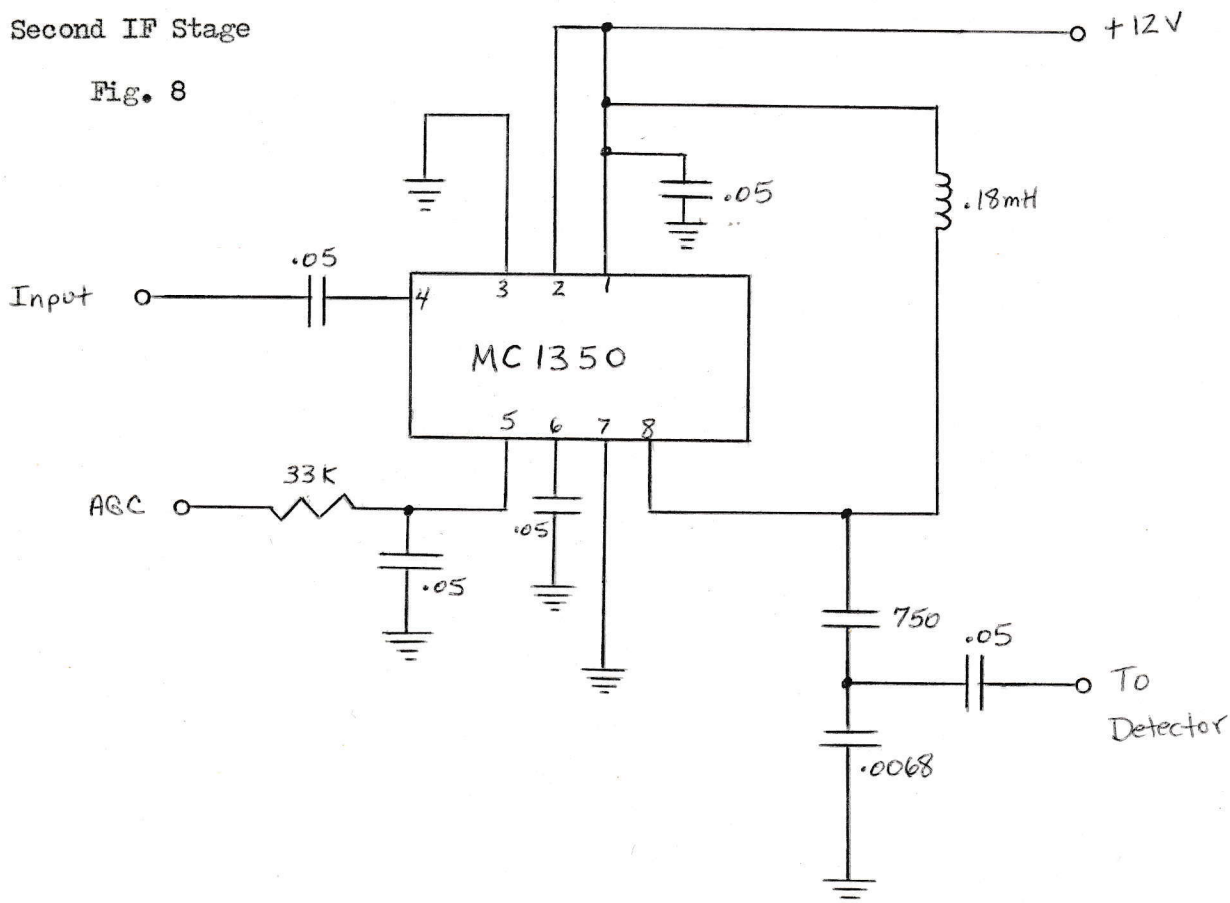

Using (29C) the output matching is found.

Select a Q of 10

$$\frac{455 \text{ kHz}}{45 \text{ kHz}} = 10 \text{ (loaded Q)}$$

$$Q_L \sqrt{\frac{R_L}{R_{in}} - 1} = \sqrt{\frac{10 \text{ K}}{125} - 1} = 8.89$$

A minimum loaded Q of 8.89 is necessary for proper operation of the matching circuit. A Q of 10 satisfies this requirement and provides an adequate margin for error

$$C_{\text{total}} = \frac{Q_L}{2(\pi)f\left(\frac{R_L}{2}\right)} = \frac{10}{2(\pi)(455 \text{ kHz})(5 \text{ K})} = 700 \text{ pF}$$

$$\frac{C_2}{C_1} = \sqrt{\frac{10 \text{ K}}{125} - 1} = 7.94 \quad X_L = X_{C \text{ tot}}$$

The matching network values are  $C_1 = 788 \text{ pF}$ ,  $C_2 = 0.00626 \text{ uF}$ , and  $L = 0.1748 \text{ mH}$ . Using these calculations as a guideline, component values which are more standard near the calculated values are chosen.

$$L = 0.18 \text{ mH}$$

$$C_1 = 750 \text{ pF}$$

$$C_2 = 0.0068 \text{ uF}$$

These component values give resonance at 456.4 kHz which is satisfactory for a Q of 10 at 455 kHz.


An automatic gain control voltage is applied to the AGC inputs of both MC1350's (Fig. 9). Gain is at a maximum for  $V_{\text{agc}} = 5$  volts and a minimum for  $V_{\text{agc}} = 6.7$  volts. The actual circuit construction of the AGC portion was found in an IF stage using devices similar to the MC1350 integrated circuits. In its configuration, the CA3160 is set for a voltage gain of 51.

The output of the device is rectified and fed back to the AGC inputs of the two stage IF amplifier system. The MC1350's have an AGC range of at least 60 dB.

The audio stage is a single LM380 audio amplifier chip which is able to deliver one watt into 8 ohms. Bypassing is used as outlined by the manufacturer.

A relatively simple power supply is used. Several different voltage levels are required; + 8 and +12 volts. One drawback of the design is that the chassis is not at true power line ground, but is actually at +12 volts with respect to ground. The complete supply is shown in Fig. 8a.

Receiver Power Supply  
Fig. 8a

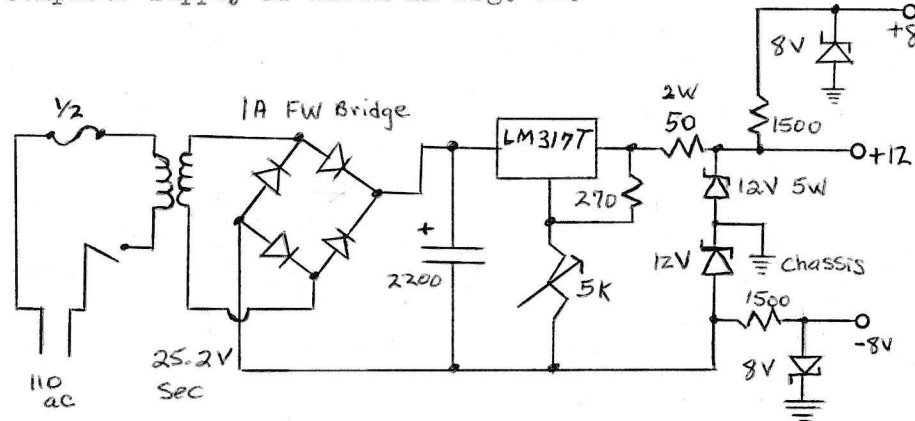

The Colpitts oscillator is contained in a separate shielded area away from the other receiver stages. All circuitry is mounted on printed circuit boards and a minimum of point-to-point wiring is used. Several wire lengths are used, however, and in cases where they are associated with a high-gain stage, bypass capacitors are used to minimize problems due to rf pickup. The complete local oscillator is illustrated in Fig. 9 and the mixer, IF, and audio stages are shown in Fig. 10.


The only problems encountered with the constructed receiver involved noise and low-level audio oscillations due to rf pickup from local AM and FM stations. Additional bypass capacitors in the affected areas resolved the problem. The tuned IF stage is adjusted to 455 kHz by tuning for optimum audio quality and the balance control on the MC1596 mixer adjusted for equal voltages on pins 1 and 4.

Overall receiver performance is more satisfactory than I imagined would be possible with the design. Dynamic performance is excellent and AGC action on the stages superb. A greater degree of selectivity would enhance the receiver's performance, but also influence its price adversely. The entire project cost approximately \$100 although several major components were already on hand.

## PARTS LIST

(2)	MPF102	(1)	T-68-15 toroid
(1)	2N2222A	(3)	T-30-2 toroid
(9)	1N914	(2)	9.1 mH RFC
(2)	MC1350	(3)	120 uH RFC
(1)	MC1596	(1)	0.18 mH RFC
(1)	CA3160	(1)	5-50 pF variable cap
(1)	9 volt zener, 1 W	(1)	3 position SPST
(2)	8.1 volt zener, 1 W	(1)	200 uA meter
(2)	12 volt zener, 1 W	(1)	13:1 gear reduction drive
(2)	100 K ohm potentiometer	(1)	25.2 V 1 amp transformer
(1)	50 K trim pot	(1)	2200 uF, 50 V electrolytic cap
(1)	1 K trim pot	(1)	SFD455 crystal filter, Murata
(1)	120 pF trimmer cap	(1)	220 UF electrolytic cap, 25 V
(1)	8"x11"x3" enclosure	(1)	47 uF electrolytic cap, 16 V

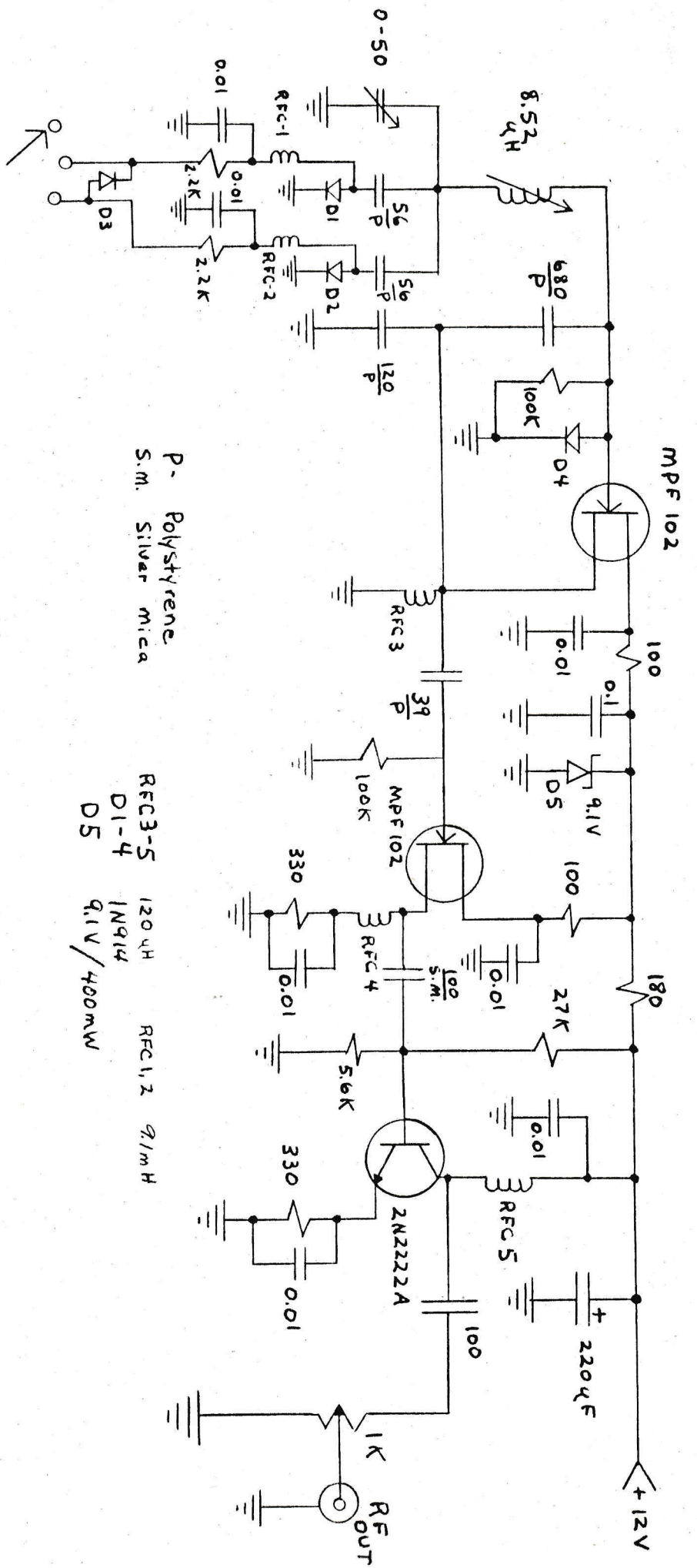Other capacitors and resistors as listed on schematic




P. Polystyrene  
S.M. Silver mica


RFC3-5 120µH  
D1-4 1N914  
D5 9.1V / 400mW  
RFC1,2 9.1mH

Fig 9  
Colpitts Oscillator



Fig. 10  
RF, IF, AUDIO  
SECTIONS

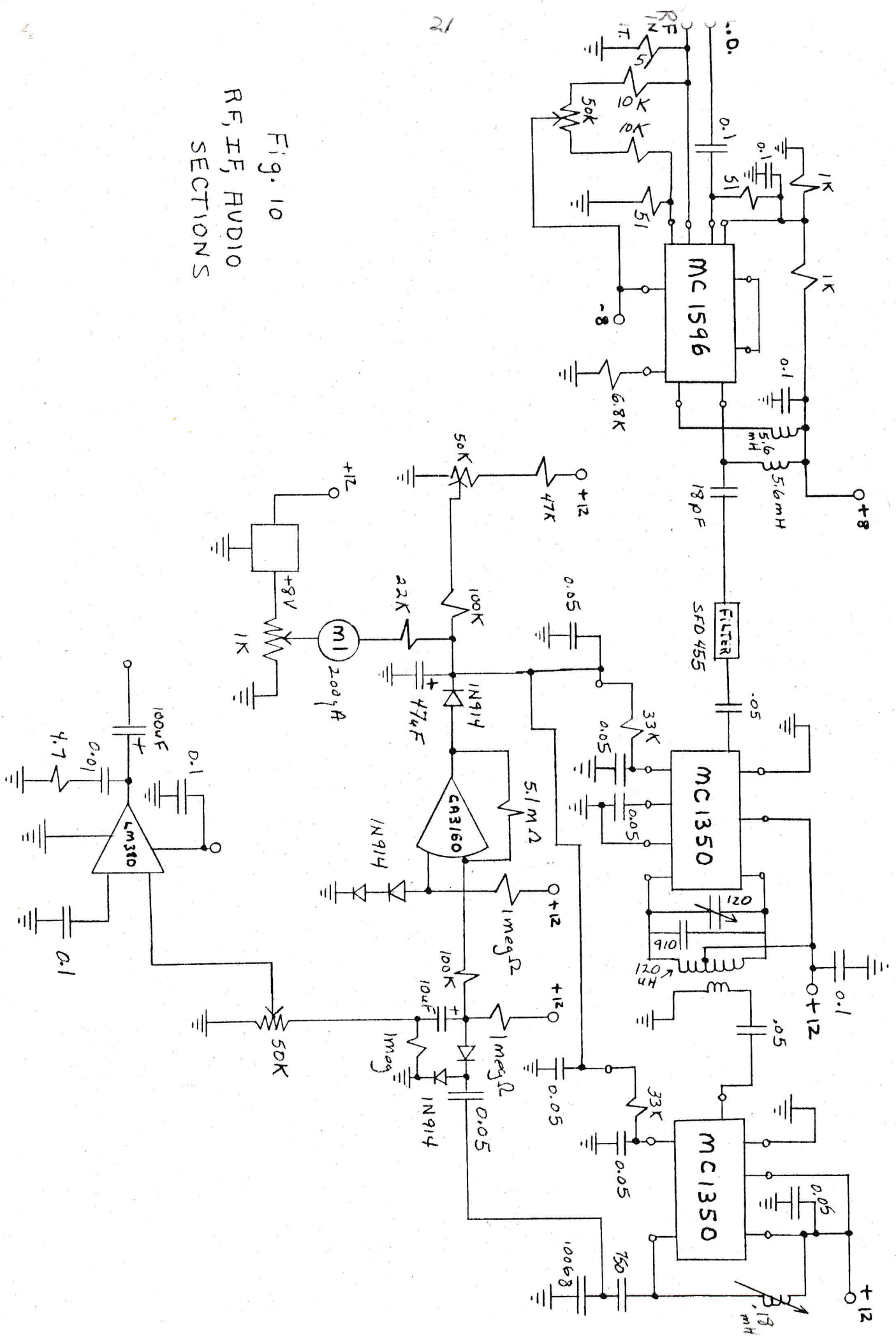

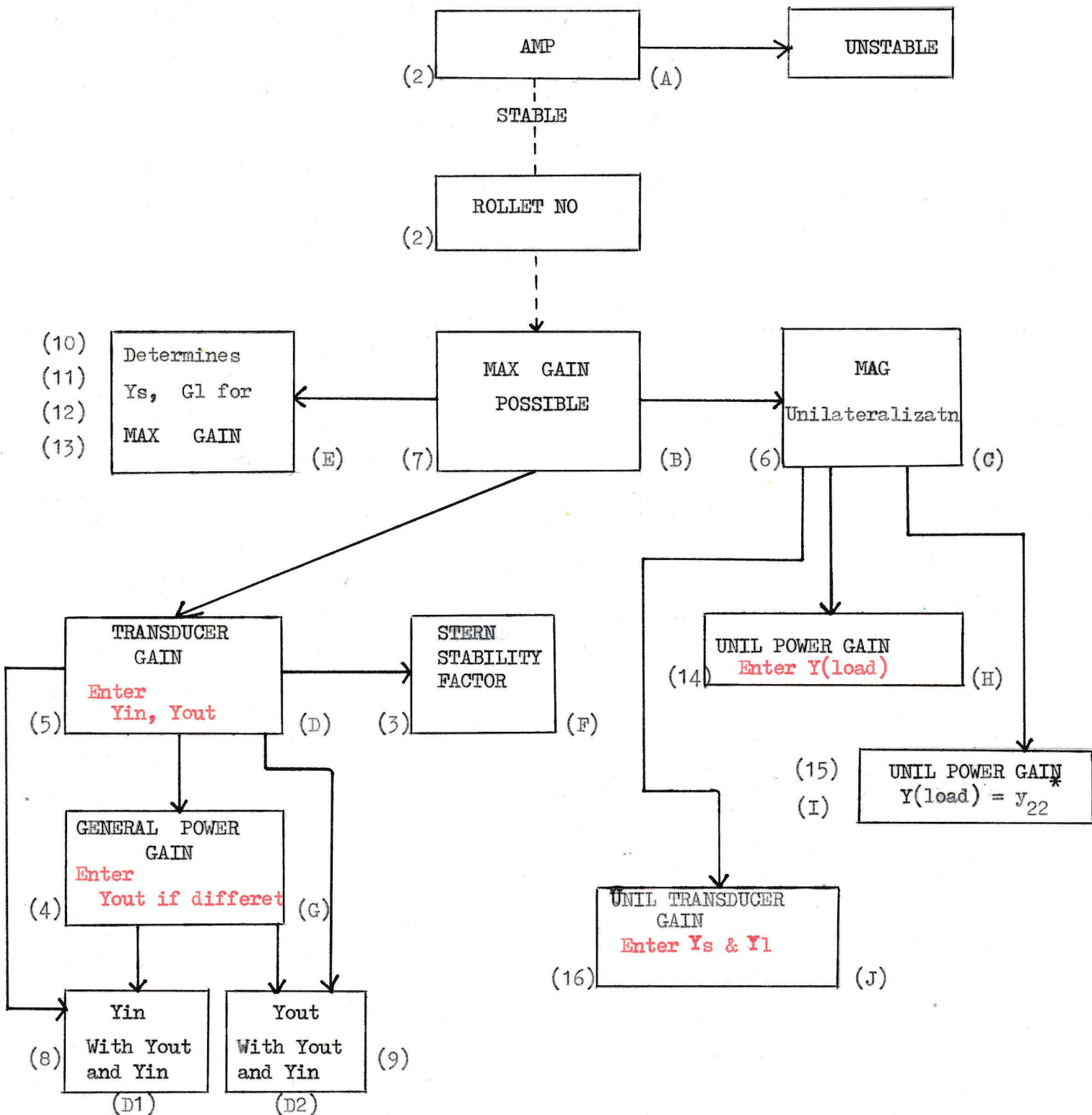

## HIGH FREQUENCY AMPLIFIER DESIGN

Lbl AMP	R00	g11	R09	B1	R18	Im(y12y21)
"Parameters"	R01	b11	R10	G in	R19	work
Aview	R02	g12	R11	B in	R20	work
Pse	R03	b12	R12	y12y21		
H Yes = 1	R04	g21	R13	angle		
Prompt	R05	b21	R14	k-Rollet		
x=0?	R06	g22	R15	work		
GTO AA	R07	b22	R16	work		
GTO HH	R08	G1	R17	Re(y12y21)		
10 RTN	RCL 12		Aview	+		STO 19
Lbl AA	60 /		RTN	R-P		R !
G11	STO 14		110 Lbl C	160 ST * 15		210 RCL 01
Prompt	1		RCL 05	R !		+
STO 00	X Y		RCL 04	ST + 16		RCL 19
B11	X Y?		R-P	RCL 16		Y in, Re
Prompt	GTO 01		x <sup>2</sup>	RCL 15		ARCL.X
STO 01	"POT UNSTABLE"		4	P-R		MHOS
G12	Aview		/	STO 15		Aview
Prompt	STOP		RCL 00	R !		Pse
20 STO 02	Lbl 01		/	STO 16		R !
B12	70 "STABLE"		RCL 06	RCL 13		Y in, Im
Prompt	Aview		120 /	170 RCL 12		220 ARCL.X
STO 03	Pse		LOG	CHS		MHOS
G21	Pse		10	P-R		Aview
Prompt	RCL 14		*	ST + 15		CF 00
STO 04	K:R=		MAG=	R !		RTN
B21	ARCL.X		ARCL.X	ST + 16		Lbl D2
Prompt	Aview		dB	RCL 16		RCL 01
STO 05	Pse		Aview	RCL 15		RCL 11
30 G22	Pse		RTN	R-P		+
Prompt	80 Lbl B		Lbl D	x <sup>2</sup>		RCL 00
STO 06	RCL 05		130 Y in, Re	180 STO 15		230 RCL 10
B22	RCL 04		Prompt	Lbl 03		+
Prompt	R-P		STO 10	RCL 05		R-P
STO 07	STO 15		Y in, Im	RCL 04		STO 15
Lbl A	RCL 03		Prompt	R-P		R !
RCL 03	RCL 02		STO 08	x <sup>2</sup>		STO 16
RCL 02	R-P		YL, Im	RCL 08		RCL 13
R-P	RCL 15		140 Prompt	*		RCL 16
40 STO 12	X Y		STO 09	RCL 10		-
R !	90 /		Lbl 02	*		RCL 12
STO 13	STO 15		RCL 01	190 4		240 RCL 15
RCL 05	RCL 14		RCL 11	*		/
RCL 04	x <sup>2</sup>		+	RCL 15		P-R
R-P	1		RCL 00	/		STO 15
ST * 12	-		RCL 10	LOG		R !
R !	SQRT		+	10		STO 16
ST + 13	CHS		R-P	**		RCL 06
RCL 13	RCL 14		150 STO 15	G-TD=		RCL 15
50 RCL 12	+		RDN	ARCL.X		-
P-R	100 RCL 15		STO 16	dB		Yout, Re
CHS	*		RCL 07	200 Aview		250 ARCL.X
RCL 00	LOG		RCL 09	RTN		Aview
RCL 06	10		+	Lbl D1		Pse
*	*		RCL 06	SF 00		RCL 07
2	GMAX=		RCL 08	GTO 11		RCL 16
*	ARCL.X			Lbl 12		-
+	dB			RCL 00		
				+		

Yout Im  
 ARCL.X  
 Aview  
 RTN  
 260 Lbl E  
 RCL 13  
 RCL 12  
 P-R  
 STO 17  
 R !  
 STO 18  
 Lbl 04  
 RCL 12  
 x<sup>2</sup>  
 270 STO 15  
 RCL 00  
 2  
 \*  
 RCL 06  
 \*  
 RCL 17  
 x<sup>2</sup>  
 x<sup>2</sup>  
 RCL 15  
 280 -  
 SQRT  
 STO 19  
 2  
 /  
 RCL 06  
 /  
 GS=  
 ARCL.X  
 MHOS  
 290 Aview  
 Pse  
 Pse  
 Lbl 05  
 RCL 18  
 2  
 /  
 RCL 06  
 /  
 STO 20  
 300 RCL 01  
 -  
 BS=  
 ARCL.X  
 MHOS  
 Aview  
 Pse  
 Pse  
 RCL 19  
 2  
 /

RCL 00  
 /  
 GL=  
 ARCL.X  
 MHOS  
 Aview  
 Pse  
 Pse  
 RCL 20  
 RCL 06  
 \*  
 RCL 00  
 /  
 RCL 07  
 -  
 BL=  
 ARCL.X  
 MHOS  
 Aview  
 330 RTN  
 Lbl F  
 RCL 00  
 RCL 10  
 +  
 RCL 08  
 RCL 06  
 +  
 \*  
 2  
 \*  
 RCL 12  
 RCL 17  
 +  
 /  
 K.FT.=  
 ARCL.X  
 Aview  
 RTN  
 Lbl G  
 Same Load?  
 Aview  
 Pse  
 Yes = 1  
 Aview  
 STOP  
 x=0?  
 GTO 10  
 Lbl 11  
 RCL 09  
 360 RCL 07  
 +  
 RCL 08  
 RCL 06  
 +  
 R-P  
 STO 15

R !  
 STO 16  
 RCL 13  
 RCL 16  
 -  
 RCL 12  
 RCL 15  
 /  
 CHS  
 P-R  
 FS? 00  
 GTO 12  
 RCL 00  
 +  
 RCL 15  
 x<sup>2</sup>  
 \*  
 STO 19  
 RCL 05  
 RCL 04  
 R-P  
 x<sup>2</sup>  
 RCL 08  
 390 \*  
 RCL 19  
 /  
 LOG  
 10  
 \*  
 G.PG.=  
 ARCL.X  
 dB  
 Aview  
 STOP  
 Lbl 10  
 Yl, Re  
 Prompt  
 STO 08  
 Yl, Im  
 Prompt  
 STO 09  
 GTO 11  
 RTN  
 Lbl H  
 LOAD, Im?  
 Prompt  
 STO 09  
 Lbl 13  
 RCL 09  
 RCL 07  
 420 +  
 RCL 03  
 +  
 RCL 08  
 RCL 06  
 +

RCL 02  
 +  
 R-P  
 STO 15  
 R !  
 STO 16  
 RCL 15  
 x<sup>2</sup>  
 RCL 00  
 \*  
 STO 19  
 Lbl 14  
 RCL 05  
 RCL 03  
 -  
 RCL 04  
 RCL 02  
 -  
 R-P  
 x<sup>2</sup>  
 STO 20  
 RCL 19  
 1/x  
 RCL 20  
 450 \*  
 RCL 08  
 \*  
 LOG  
 10  
 \*  
 G.PG=  
 ARCL.X  
 dB  
 Aview  
 RTN  
 Lbl I  
 RCL 00  
 RCL 02  
 +  
 4  
 \*  
 RCL 06  
 RCL 02  
 +  
 \*  
 1/x  
 RCL 20  
 \*  
 LOG  
 10  
 \*  
 GU.=  
 ARCL.X  
 dB  
 480 Aview

RTN	G.TU.=	R-P	ST + 08
Lbl J	ARCL.X	CHS	-1
GS Re	dB	STO 20	ST * 20
Prompt	Aview	R !	RCL 19
STO 10	RTN	RCL 19	RCL 18
GS Im		-	P-R
Prompt	Lbl HH	RCL 20	STO 18
STO 11	540 H11 Re	RCL 18	R !
Same Load?	Prompt	/	STO 19
Aview	STO 10	P-R	RCL 08
Pse	H11 Im	STO 02	RCL 20
Yes = 1	Prompt	R !	P-R
Prompt	STO 11	STO 03	650 ST + 18
x=0?	H12 Re	Lbl 22	R !
GTO 16	Prompt	RCL 15	ST + 19
GTO 15	STO 12	RCL 14	RCL 19
Lbl 16	H12 Im	R-P	RCL 18
GL Re	Prompt	RCL 18	R-P
Prompt	STO 13	/	STO 18
STO 08	H21 Re	STO 18	R !
GL Im	Prompt	R !	STO 19
Prompt	STO 14	RCL 19	RCL 11
STO 09	H21 Im	-	RCL 10
GTO 15	Prompt	RCL 18	R-P
Lbl 15	STO 15	P-R	ST / 18
RCL 01	H22 Re	610 STO 04	R !
RCL 03	Prompt	R !	ST-19
+	STO 16	STO 05	RCL 19
510 +	560 H22 Im	Lbl 23	RCL 18
RCL 00	Prompt	RCL 11	P-R
RCL 02	STO 17	RCL 10	STO 06
+	Lbl 20	R-P	R !
RCL 10	RCL 11	STO 18	STO 07
+	RCL 10	R !	GTO AA
R-P	R-P	STO 19	RTN
RCL 15	1/x	RCL 17	673 END
$\frac{*}{2}$	X Y	RCL 16	
x	CHS	R-P	
STO 16	X Y	ST * 18	
Lbl 16	P-R	R !	
RCL 10	STO 00	ST + 19	
RCL 08	R !	Lbl 24	
*	STO 01	RCL 13	
4	Lbl 21	RCL 12	
*	RCL 11	R-P	
RCL 20	RCL 10	STO 20	
*	R-P	R !	
RCL 16	580 STO 18	STO 08	
/	R !	RCL 15	
LOG	STO 19	RCL 14	
10	RCL 13	R-P	
*	RCL 12	ST * 20	
		R !	

## GLOSSARY OF TERMS

C	Linville Stability Factor
kr	Rollet Stability Factor
K, k	Stern Stability Factor
G <sub>s</sub>	Real part of source admittance
G <sub>l</sub>	Real part of load admittance
B <sub>s</sub>	Imaginary part of source admittance
B <sub>l</sub>	Imaginary part of load admittance
g <sub>ij</sub>	Real part of $y_{ij}$
b <sub>ij</sub>	Imaginary part of $y_{ij}$
Y <sub>l</sub>	Complex load admittance
Y <sub>s</sub>	Complex source admittance
*	Conjugate
Y <sub>in</sub>	Input admittance
Y <sub>out</sub>	Output admittance

## REFERENCES

1. Carson, Ralph S., High-Frequency Amplifiers, John Wiley & Sons, New York, 1975.
2. Motorola Inc., Motorola RF Data Manual, 1981.
3. DeMaw, M.F. "Doug" , Ferromagnetic Core Design & Application Handbook, Prentice-Hall, Inc., Englewood Cliffs, New Jersey, 1981.
4. American Radio Relay League, The Radio Amateurs Handbook, 1979.
5. Alley, Charles L., Kenneth W. Atwood, Electronic Engineering, Third Edition, John Wiley & Sons, New York, 1973.